

Homework 8

The sequence 01111110 is a flag used in a message communications network that represents the beginning of a message. This flag must be unique. As a consequence, at most five 1's in sequence may appear anywhere else in the message. Since this is unrealistic for normal message content, a trick called zero-insertion is used. The normal message, which can contain strings of 1's longer than 5, enters input X of a sequential zero-insertion circuit given below:

The circuit has two outputs Z and S. When a sixth 1 in sequence appears on X, a 0 is inserted into the stream of outputs appearing on Z and the output S = 1 indicating that a zero-insertion has happened. Zero-insertion is illustrated by the following example sequences:


Message sequence on X: 011111**1**0011111**1**1100001011110101

Output sequence on Z: 011111**0**0011111**0**1100001011110101

Zero-insertion indicator on S: 000000**1**000000**0**1000000000000000

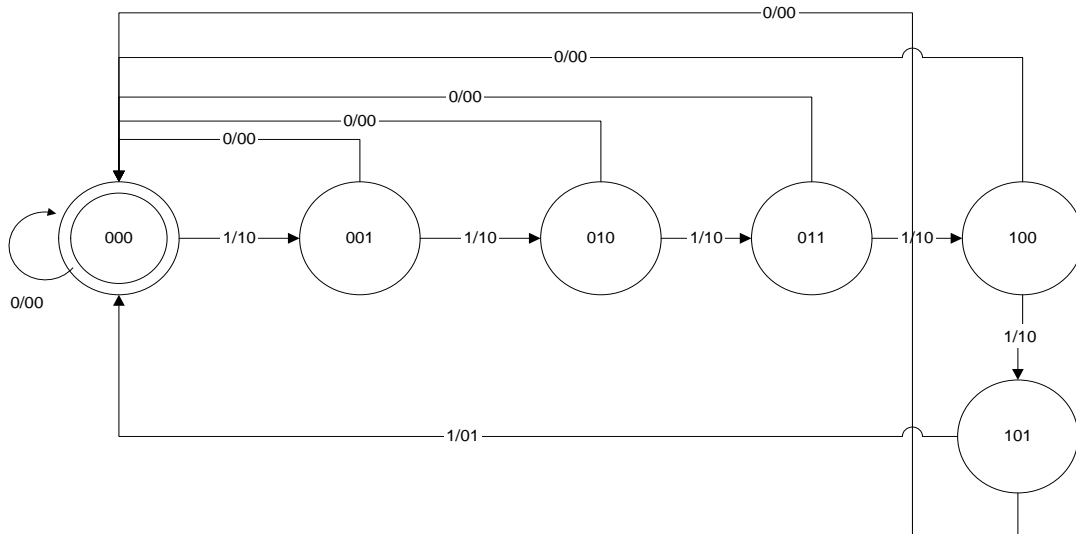
Task: Design the zero-insertion circuit above following the 9-step design procedure given in Lecture 10 using SR Flip-Flops and logic gates.

We have to insert 1 zero every time we recognize 5 ones in the sequence and another 1 is waiting at input. We can make a state machine of this situation but it is clear that we need 6 states to remember the zero to five ones, which means we need 3 bits to encode this. This also means we need 3 flip flops.




Now that we have all the needed tables, we can construct our Boolean equations and simplify them with k-maps.

S1)

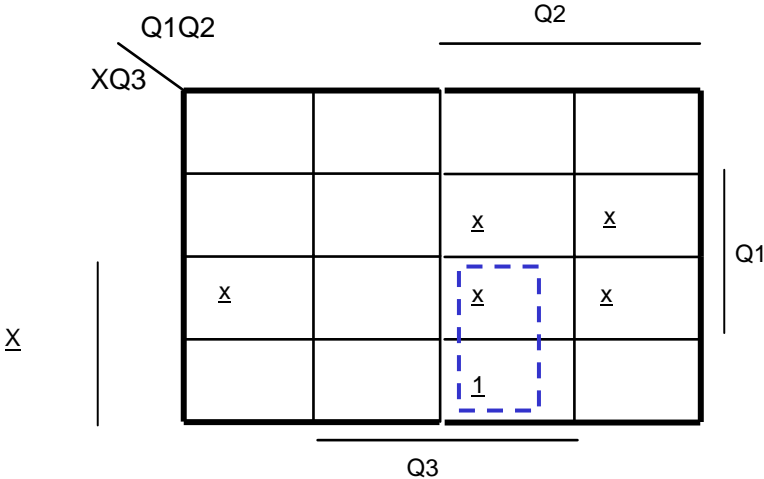


$$S1 = XQ_2Q_3$$

R1)

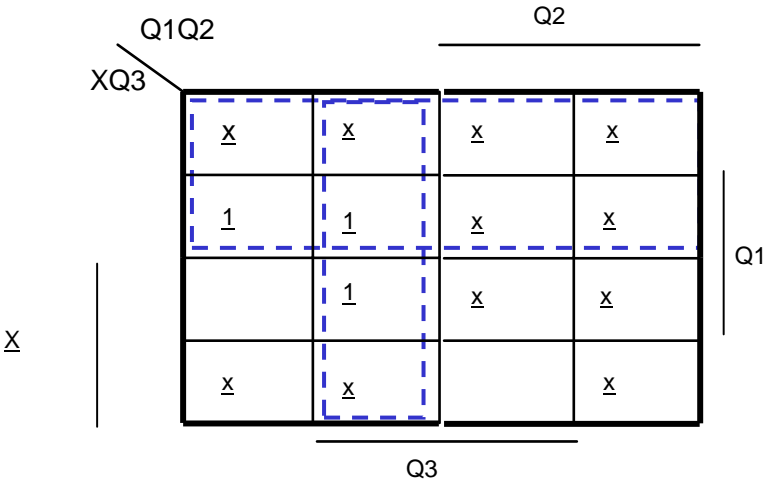


$$R1 = X' + Q_2'Q_3$$

S2)

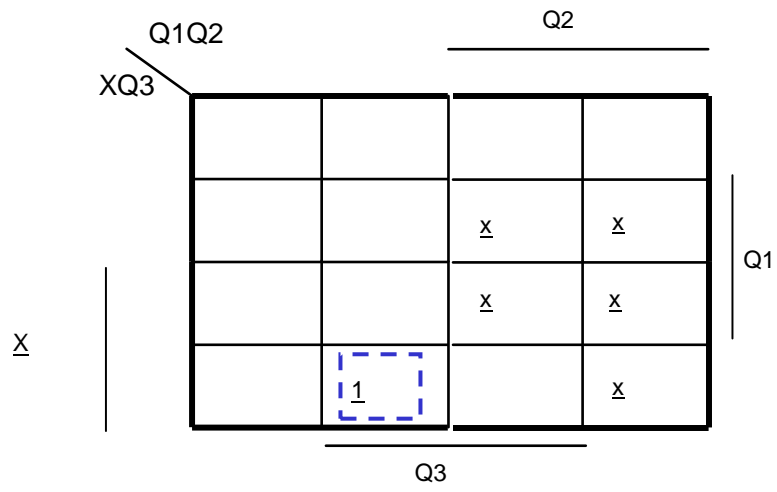


$$S2 = XQ_1'Q_2'Q_3$$

R2)

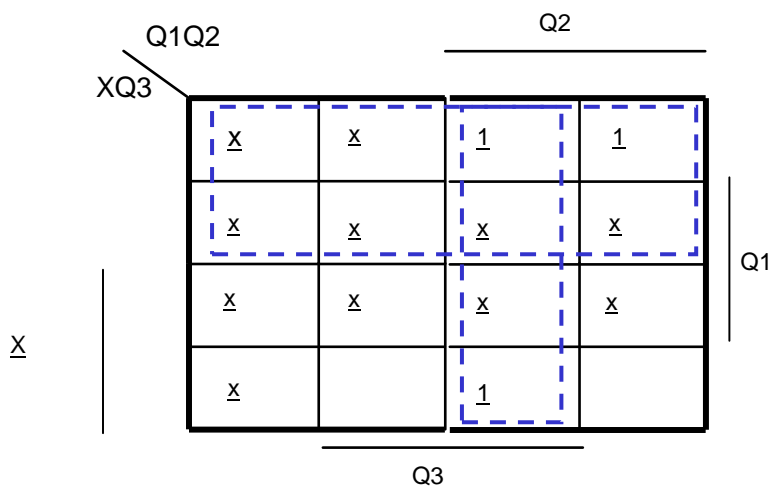


$$R2 = X' + Q_2Q_3$$

S3)

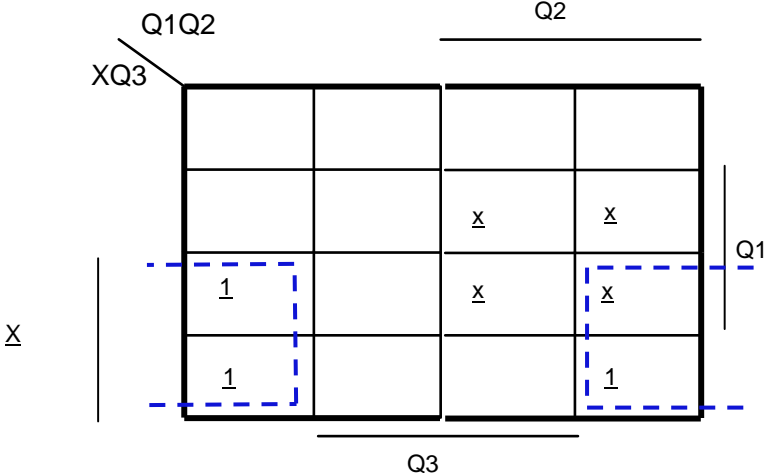


$S3 = XQ_3'$

R3)

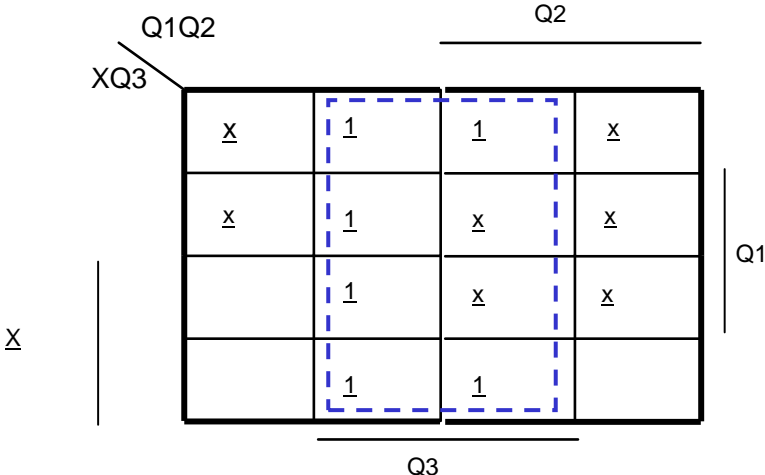


$R3 = Q_3$

Z)

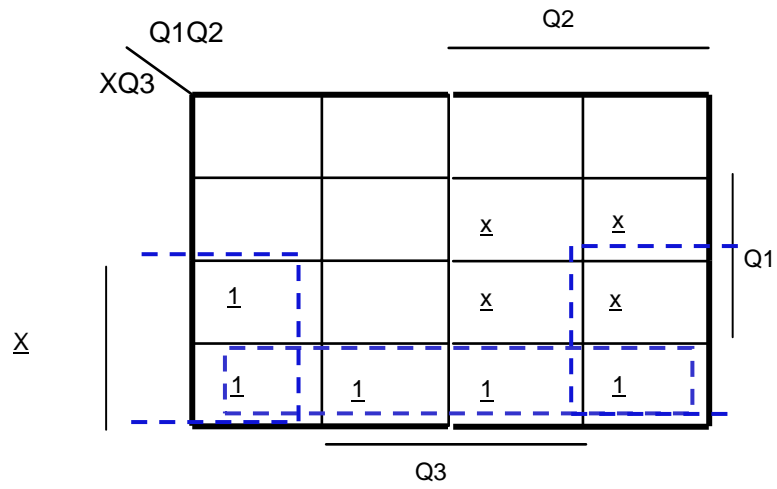

$$Z = XQ_1' + XQ_3'$$

S)

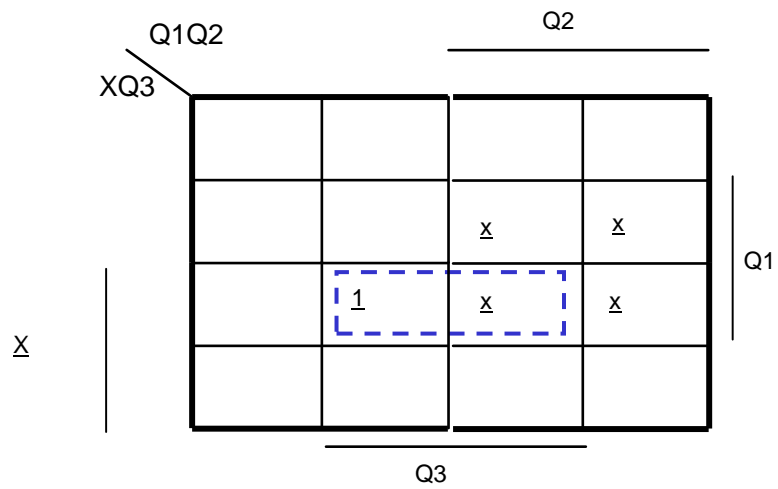

$$S = XQ_1Q_3$$

The schematic of our functions

