

Homework 6

1) A sequential circuit with two flip-flops A and B, one input X, and one output Z is specified by the following equations:

$$A(t+1) = X'A(t) + XB(t)$$

$$B(t+1) = X'A(t)'$$

$$Z = XA(t) + XB(t)'$$

Transform and implement the sequential circuit **as Moore finite state machine (FSM)**:

- (a) Draw the logic diagram of the Moore FSM;
- (b) Derive the state table of the Moore FSM;
- (c) Derive the state diagram of the Moore FSM;