

# Homework 7

**Task 1)** Given SR Flip-Flop, design:

- a) JK Flip-Flop
- b) T Flip-Flop

**Task 2)** Given JK Flip-Flop, design:

- a) SR Flip-Flop
- b) D Flip-Flop

**Show the whole design procedure not only the final result!**