

# Combinational Logic Design

---

## Combinational Functions and Circuits




# Overview

---

- Combinational Circuits
- Design Procedure
  - Generic Example
  - Example with don't cares: BCD-to-SevenSegment converter
- Binary Decoders
  - Functionality
  - Circuit Implementation with Decoders
  - Expansion
- Multiplexers (MUXs)
  - Functionality
  - Circuit Implementation with MUXs
  - Expansions
 
# Combinational Circuits

- A combinational circuit consists of logic gates




- The circuit outputs, at any time, are determined by combining the values of the inputs
- For  $n$  inputs, there are  $2^n$  possible binary input combinations
- For each combination, there is one possible binary value on each output
- Hence, a combinational circuit can be described by:
  - Truth Table
    - lists the output values for each combination of the inputs
  - $m$  Boolean functions, one for each output
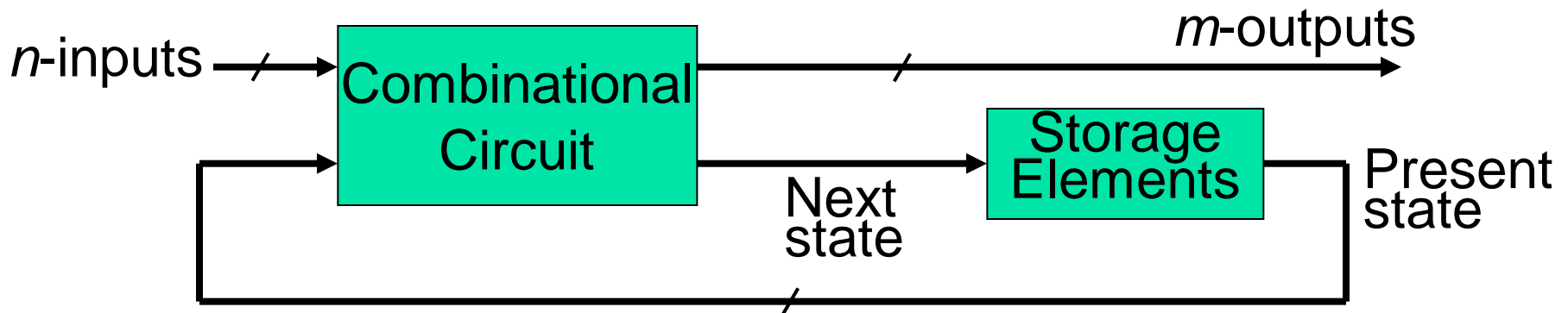
# Combinational vs. Sequential Circuits

- Combinational circuits are **memory-less!**
  - Thus, the output values depend ONLY on the current input values



- Sequential circuits consist of **combinational logic** as well as **memory (storage) elements!**
  - Memory elements used to store certain circuit states
  - Outputs depend on **BOTH** current input values and previous input values kept in the storage elements





# Combinational Circuit Design

---

- ***Design*** of a combinational circuit is the development of a circuit from a description of its function
- It starts with a problem specification
- It produces
  - a logic diagramOR
  - set of Boolean equations that represent the circuit



# Design Procedure

---

Consists of 5 major steps:

1. Determine the required number of inputs and outputs and assign variables to them
2. Derive the truth table that defines the required relationship between inputs and outputs
3. Obtain and simplify the Boolean functions
  - Use K-maps, algebraic manipulation, CAD tools, etc.
  - **Consider any design constraints** (area, delay, power, available libraries, etc.)
4. Draw the logic diagram
5. Verify the correctness of the design



# Design Example

---

- Design a combinational circuit with 4 inputs that generates a 1 when
  - the # of 1s on the inputs equals the # of 0s



OR

- the # of 1s on the inputs equals to 1
- Constraints: Use only 2-input NAND gates!

**Let us do it on the black board**
  
# Another Example: BCD-to-Seven-Segment Converter

- Converts BCD code to Seven-Segment code
  - Used to display numeric info on 7 segment display
  - Input is a 4-bit BCD code (w, x, y, z)
  - Output is a 7-bit code (a,b,c,d,e,f,g)



- Example:
  - Input:  $0000_{\text{BCD}}$
  - Output:  $1111110$   
( $a=b=c=d=e=f=1, g=0$ )




# BCD-to-Seven-Segment (cont.)

## Truth Table

Digit	wxyz	abcdefg
0	0000	1111110
1	0001	0110000
2	0010	1101101
3	0011	1111001
4	0100	0110011
5	0101	1011011
6	0110	X011111
7	0111	11100X0

Digit	wxyz	abcdefg
8	1000	1111111
9	1001	111X011
	1010	XXXXXXXX
	1011	XXXXXXXX
	1100	XXXXXXXX
	1101	XXXXXXXX
	1110	XXXXXXXX
	1111	XXXXXXXX

??

 

Continue the design at home ...



# Design Procedure for Complex Circuits

---

- In general, digital systems are complex and sophisticated circuits
  - A circuit may consist of **millions of gates!**
- **Impossible** to design each and every circuit from scratch using the procedure you have just seen
- There is no formal procedure to design complex digital circuits!

**How to design complex digital circuits?**



# Design Procedure for Complex Circuits

---

- Fortunately, complex digital circuits can be implemented as **composition of smaller and simpler circuits**
- These smaller and simpler circuits are fundamental and we call them **basic functional blocks**
- Basic functional blocks can be designed using the procedure you have just seen!
- **Reuse** basic functional blocks to design new circuits
- Use **Design Hierarchy**
- Use **Computer-Aided Design (CAD)** tools
  - Schematic Capture tools
  - Hardware Description Languages (HDL)
  - Logic Simulators
  - Logic Synthesizers

**More details will be given at the Hands-on tutorials!**



# Basic Functional Blocks

---


- **Combinational Functional Blocks**
  - Logic Gates
  - Code Converters
  - **Binary Decoders** and Encoders
  - **Multiplexers** and Demultiplexers
  - Programmable Logic Arrays
  - Binary Adders and Subtractors
  - Binary Multipliers and Dividers
  - Shifters, Incrementors and Decrementors
- **Sequential Functional Blocks**
  - Flip-Flops and Latches
  - Registers and Counters
  - Sequencers
  - Micro-programmed Controllers
- **Memories**

# Binary Decoder

- A combinational circuit that converts an **n**-bit binary number to a unique  **$2^n$** -bit **one-hot code!**
  - Circuit is called ***n-to- $2^n$*  decoder**
  - For each input combination only one unique output is 1 (one-hot code)!

- Enable signal (**E**)  
if **E = 0** then  
**all** outputs are **0**  
else

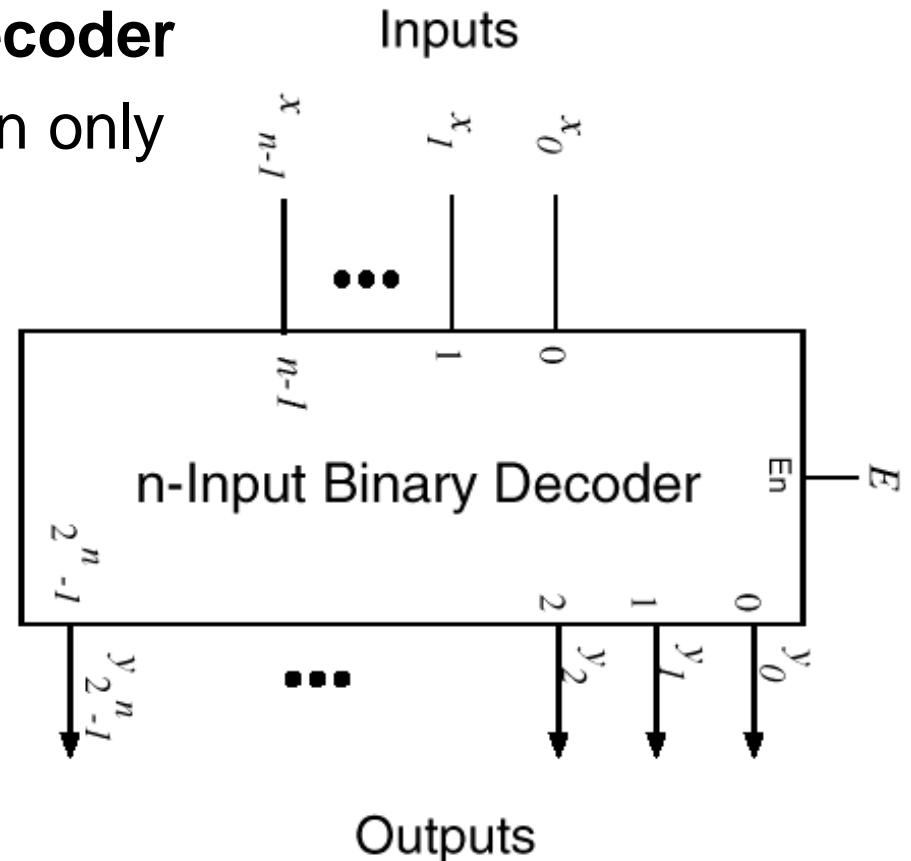
$$y_j = f(x_0, x_1, \dots, x_{n-1})$$
$$(j = 0..2^n-1)$$



# 1-to-2 Decoder

- 1-to-2 Decoder without Enable signal

Logic Symbol

 


Truth Table and Equations

A	D <sub>0</sub>	D <sub>1</sub>
0	1	0
1	0	1


$$D_0 = A'$$

$$D_1 = A$$

Logic Circuit

 


- 1-to-2 Decoder with Enable signal

 

E	A	D <sub>0</sub>	D <sub>1</sub>
0	0	0	0
0	1	0	0
1	0	1	0
1	1	0	1


$$D_0 = EA'$$

$$D_1 = EA$$

 

# 2-to-4 Decoder

## Logic Symbol

 

## Truth Table and Equations

$A_1$	$A_0$		$D_0$	$D_1$	$D_2$	$D_3$
0	0		1	0	0	0
0	1		0	1	0	0
1	0		0	0	1	0
1	1		0	0	0	1

$$D_0 = A_1'A_0'$$


$$D_1 = A_1'A_0$$

$$D_2 = A_1A_0'$$



$$D_3 = A_1A_0$$

**All minterms of 2 variables**

## Logic Circuit


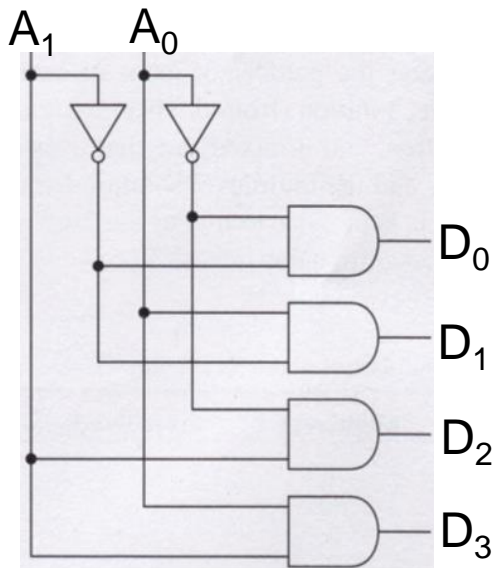


## 2-to-4 Decoder with Enable

  

# 3-to-8 Decoder

Logic Symbol

  


Truth Table

$A_2$	$A_1$	$A_0$		$D_0$	$D_1$	$D_2$	$D_3$	$D_4$	$D_5$	$D_6$	$D_7$
0	0	0		1	0	0	0	0	0	0	0
0	0	1		0	1	0	0	0	0	0	0
0	1	0		0	0	1	0	0	0	0	0
0	1	1		0	0	0	1	0	0	0	0
1	0	0		0	0	0	0	1	0	0	0
1	0	1		0	0	0	0	0	1	0	0
1	1	0		0	0	0	0	0	0	1	0
1	1	1		0	0	0	0	0	0	0	1

**Notice: D0 to D7 represent all minterms of 3 variables.**



# 3-to-8 Decoder (Logic Circuit)

 


**D0 to D7 are  
all minterms  
of 3 variables!**

# $n$ -to- $2^n$ Decoder (generalization)

- $n$  inputs,  $A_0, A_1, \dots, A_{n-1}$ , are decoded into  $2^n$  outputs,  $D_0$  through  $D_{2^n-1}$ .
- Each output  $D_j$  represents **one of the minterms** of the  $n$  input variables
- $D_j = 1$  when the binary number  $(A_{n-1} \dots A_1 A_0) = j$ 
  - Shorthand:  $D_j = m_j$
- The outputs are *mutually exclusive*
  - exactly one output has the value 1 at any time
  - the others are 0
- Due to the above properties, an **arbitrary** Boolean function of  $n$  variables can be **implemented** with  $n$ -to- $2^n$  Decoder and OR gates!
 
# Implementing Boolean Functions using Decoders

- **Select** outputs of a decoder that implement minterms included in the Boolean function
- **Make** a logic **OR** of the selected outputs
- **Example:**
  - Implement Boolean function  $F(W,X,Y,Z) = \Sigma m(1,5,6,13,15)$
  - $F$  is a function of 4 variables  $\rightarrow$  we use 4-to-16 Decoder
- **Any combinational circuit can be constructed using decoders and OR gates!**  
**Why?**




# Another Example: Implementing a Binary Full Adder using a Decoder

- Binary Full Adder has 3 inputs and 2 outputs:
  - Inputs: two bits to be added ( $b_1$  and  $b_0$ ) and a carry-in ( $C_{in}$ )
  - Outputs: sum ( $S = b_0 + b_1 + C_{in}$ ) and carry-out ( $C_{out}$ )
- Logic Functions:

$C_{in}$	$b_1$	$b_0$	<b>S</b>	<b><math>C_{out}</math></b>
0	0	0	<b>0</b>	<b>0</b>
0	0	1	<b>1</b>	<b>0</b>
0	1	0	<b>1</b>	<b>0</b>
0	1	1	<b>0</b>	<b>1</b>
1	0	0	<b>1</b>	<b>0</b>
1	0	1	<b>0</b>	<b>1</b>
1	1	0	<b>0</b>	<b>1</b>
1	1	1	<b>1</b>	<b>1</b>

$$S(C_{in}, b_1, b_0) = \sum m(1, 2, 4, 7)$$

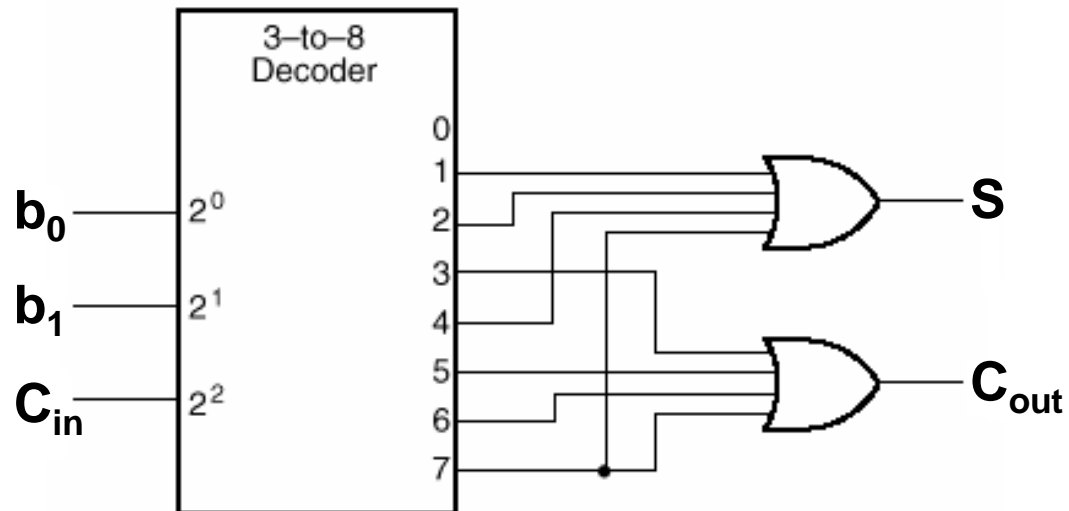
$$C_{out}(C_{in}, b_1, b_0) = \sum m(3, 5, 6, 7)$$



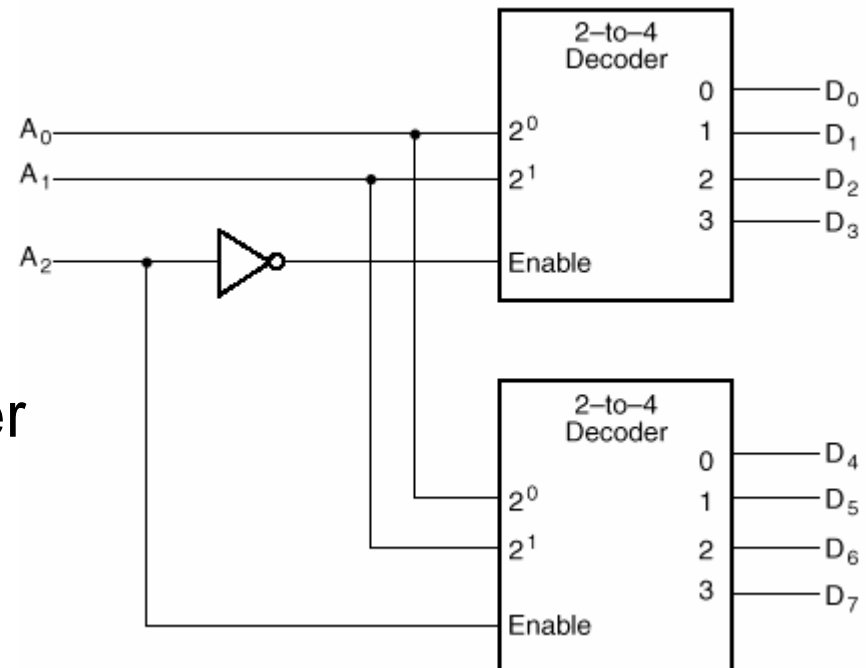
# Decoder Expansions

- **Larger** decoders can be constructed using a number of smaller ones
- Use **composition** of smaller decoders to construct larger decoders
- Example:

- Given: 2-to-4 decoders
- Required: 3-to-8 decoder
- Solution: Each decoder realizes half of the minterms  
Enable selects which decoder is active:
  - $A_2 = 0$ : enable top decoder
  - $A_2 = 1$ : enable bottom decoder



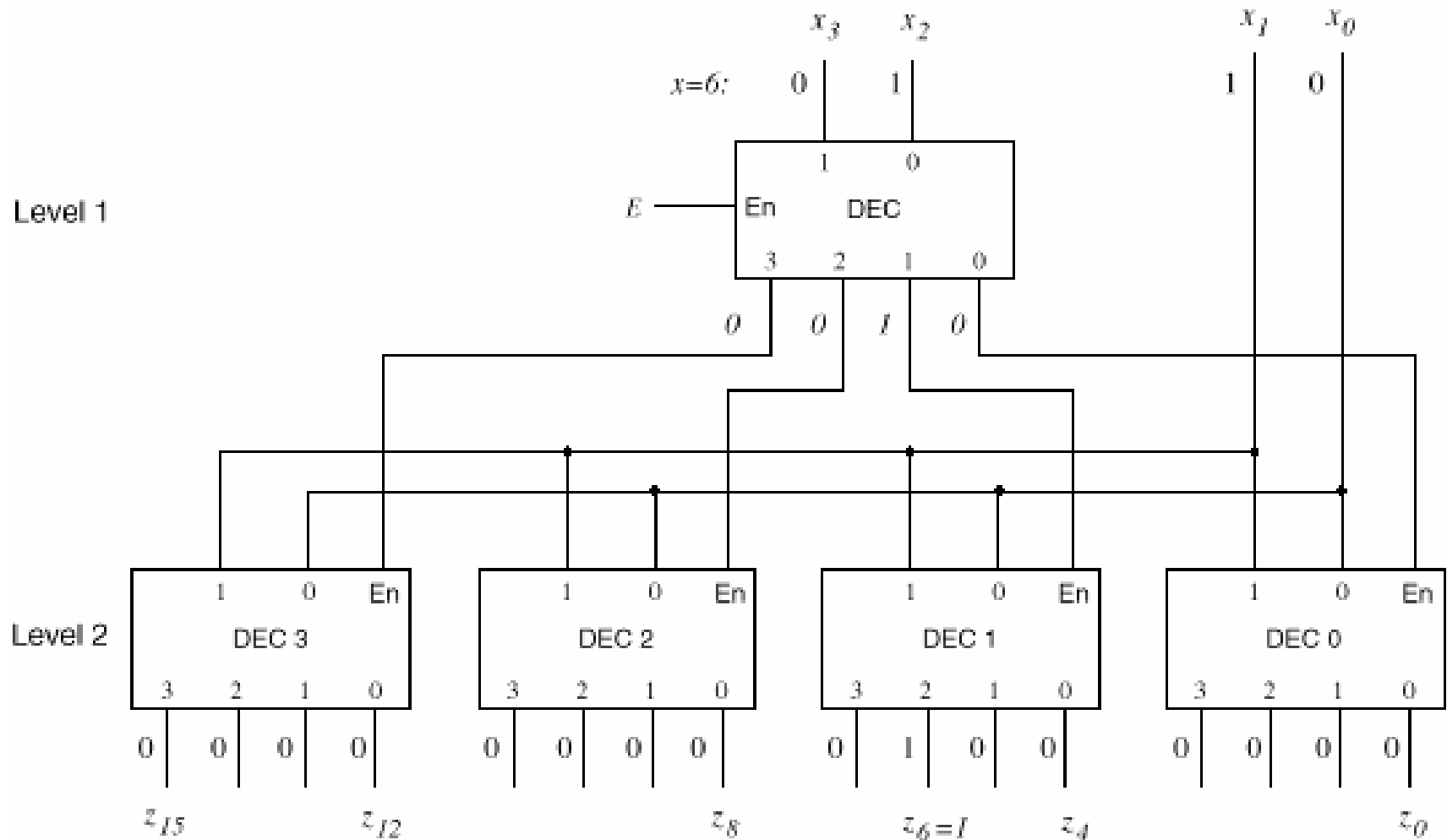
# 4-to-16 Decoder with 2-to-4 Decoders: Tree Composition of Decoders



 
# Multiplexer (MUXs)

- **Selects** one of many input data lines and directs it to a single output line
- Selection controlled by
  - set of input lines
  - whose # depends on the # of the data input lines
- A  **$2^n$ -to-1 multiplexer** has
  - $2^n$  data input lines
  - 1 output line
  - $n$  selection lines




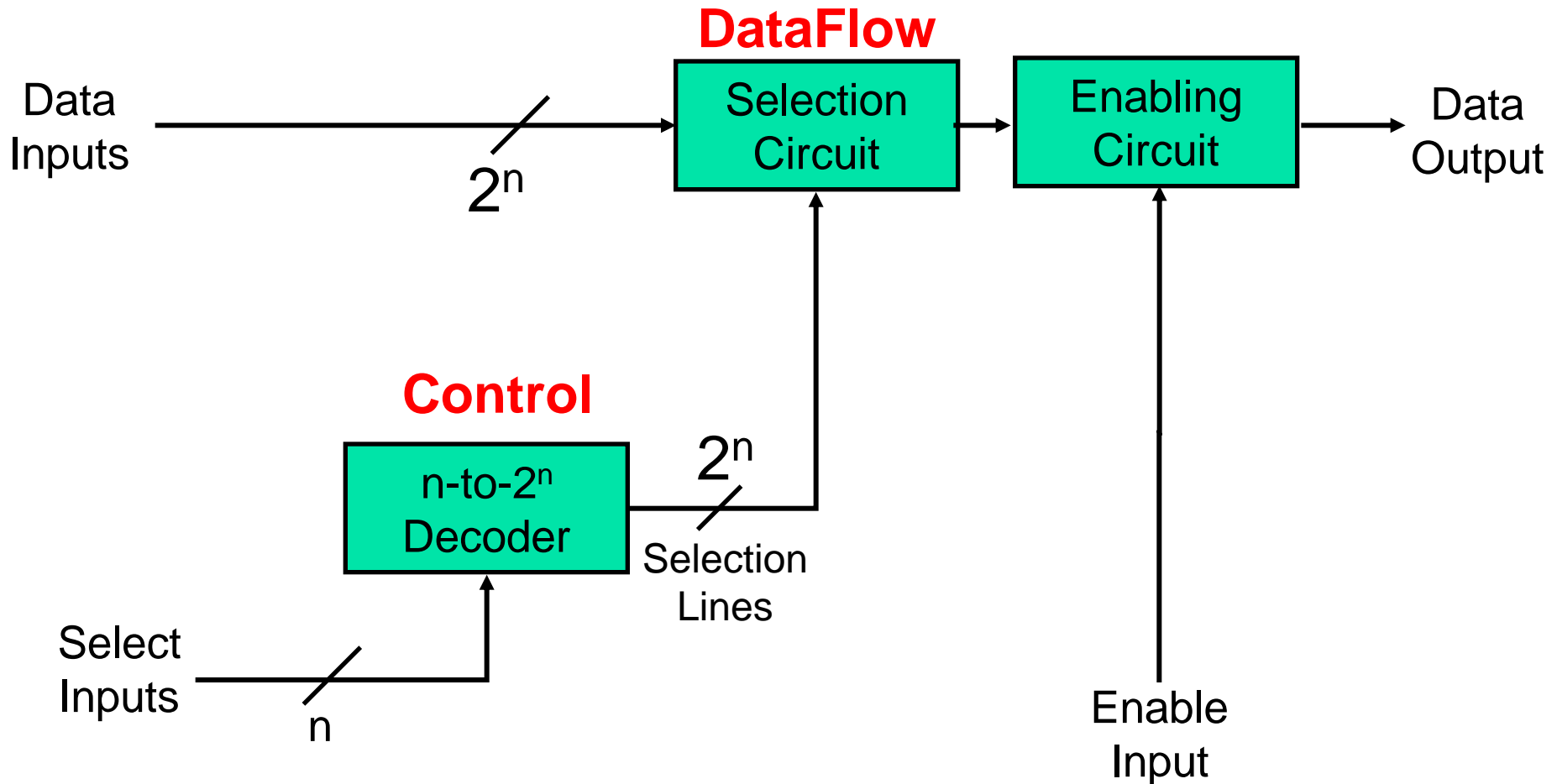
# $2^n$ -to-1 Multiplexer (General Structure)





# 2-to-1 Multiplexer

## Logic Symbol

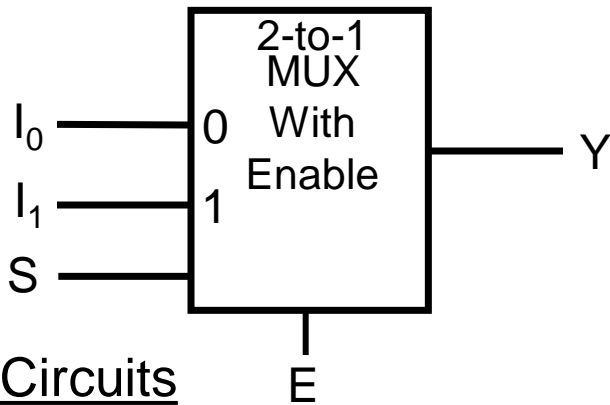 


## Truth Tables (compact and full)

S	Y
0	$I_0$
1	$I_1$



S	$I_0$	$I_1$	Y
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

## K-map and Equation

 


$$Y = S I_1 + S' I_0$$

## Logic Circuits

 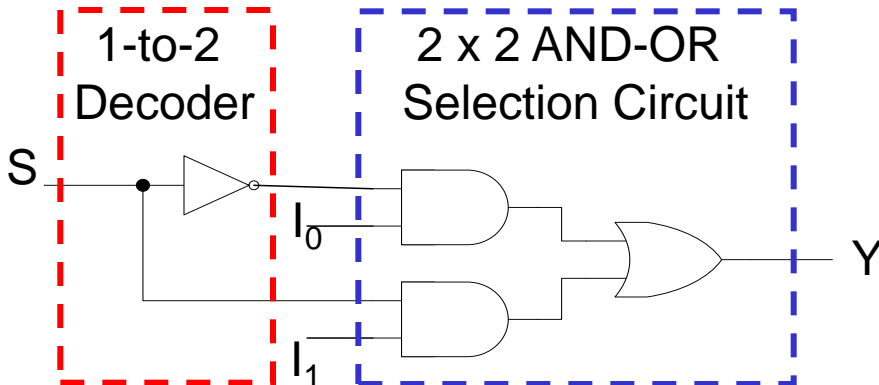

# 4-to-1 Multiplexer without Enable

Logic Symbol

 


Compact Truth Tables

S <sub>1</sub>	S <sub>0</sub>	Y
0	0	I <sub>0</sub>
0	1	I <sub>1</sub>
1	0	I <sub>2</sub>
1	1	I <sub>3</sub>

Equation


$$Y = S_1'S_0'I_0 + S_1'S_0I_1 + S_1S_0'I_2 + S_1S_0I_3$$

Logic Circuit

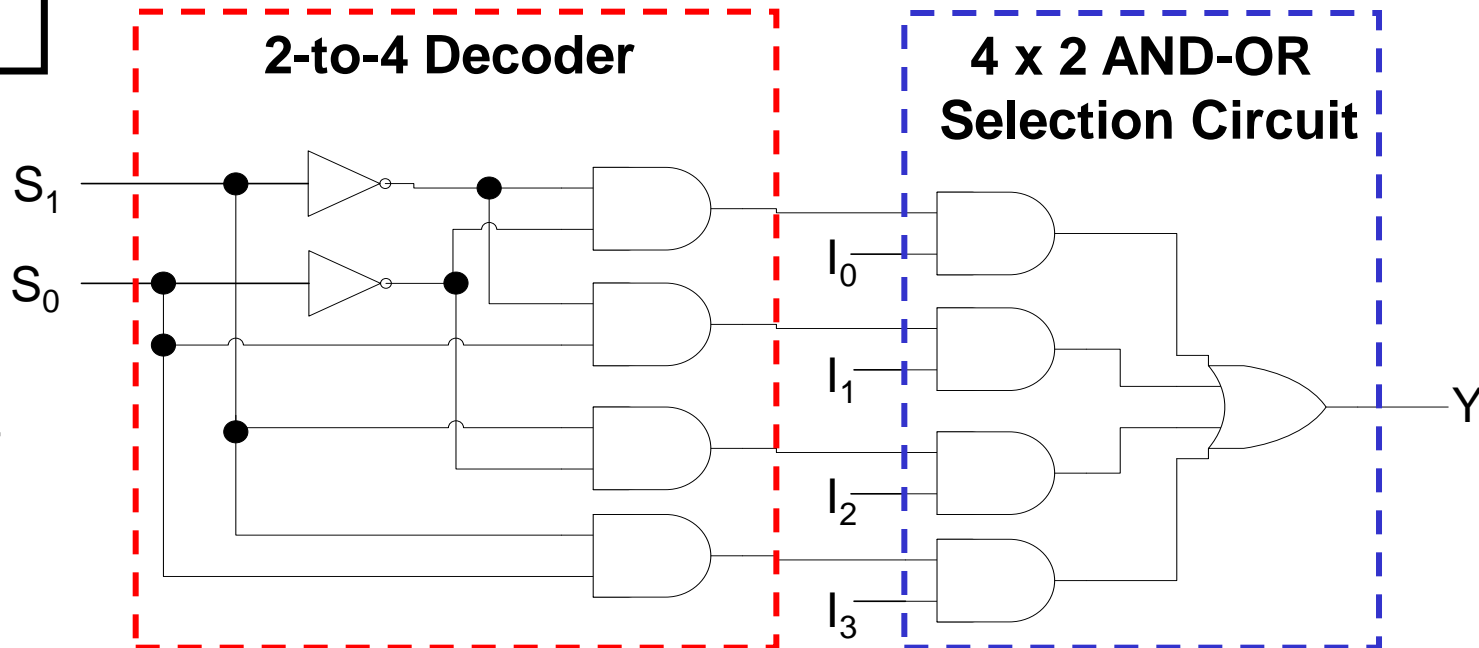

# 4-to-1 Multiplexer with Enable

Logic Symbol

 


Compact Truth Tables

E	S <sub>1</sub>	S <sub>0</sub>	Y
1	0	0	I <sub>0</sub>
1	0	1	I <sub>1</sub>
1	1	0	I <sub>2</sub>
1	1	1	I <sub>3</sub>
0	x	x	0


Equation

$$Y = E \cdot (S_1' S_0' I_0 + S_1' S_0 I_1 + S_1 S_0' I_2 + S_1 S_0 I_3)$$

Logic Circuit

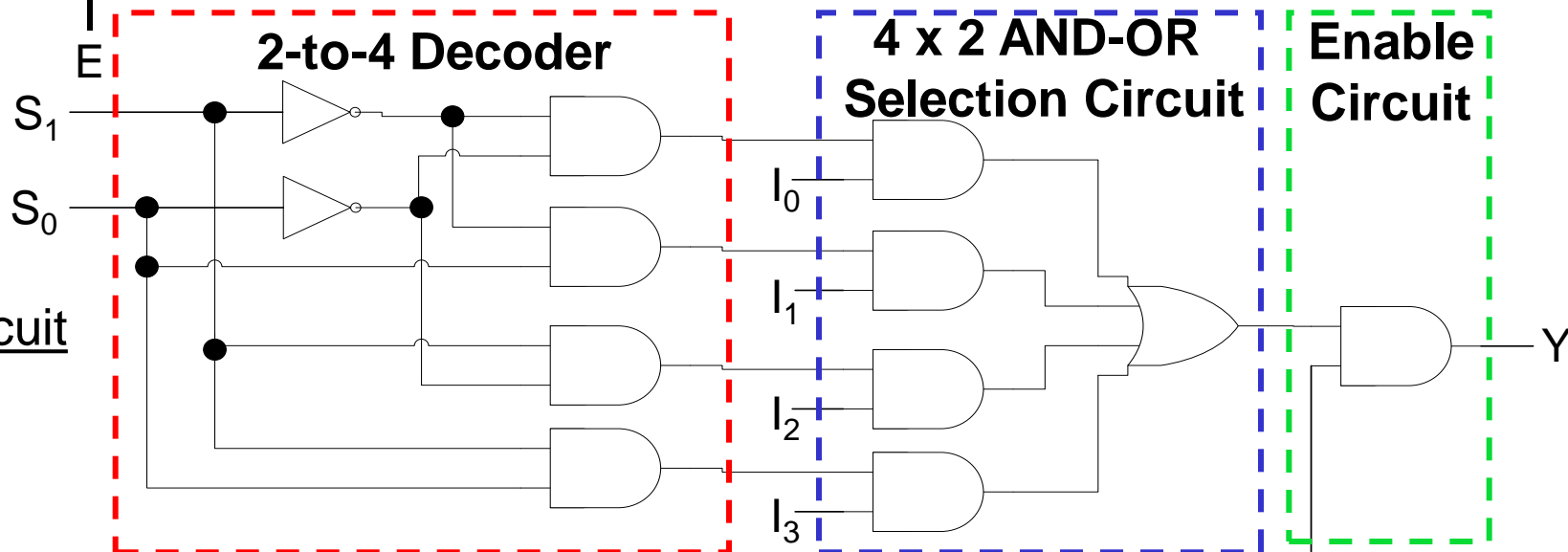


# 2<sup>n</sup>-to-1 Multiplexer

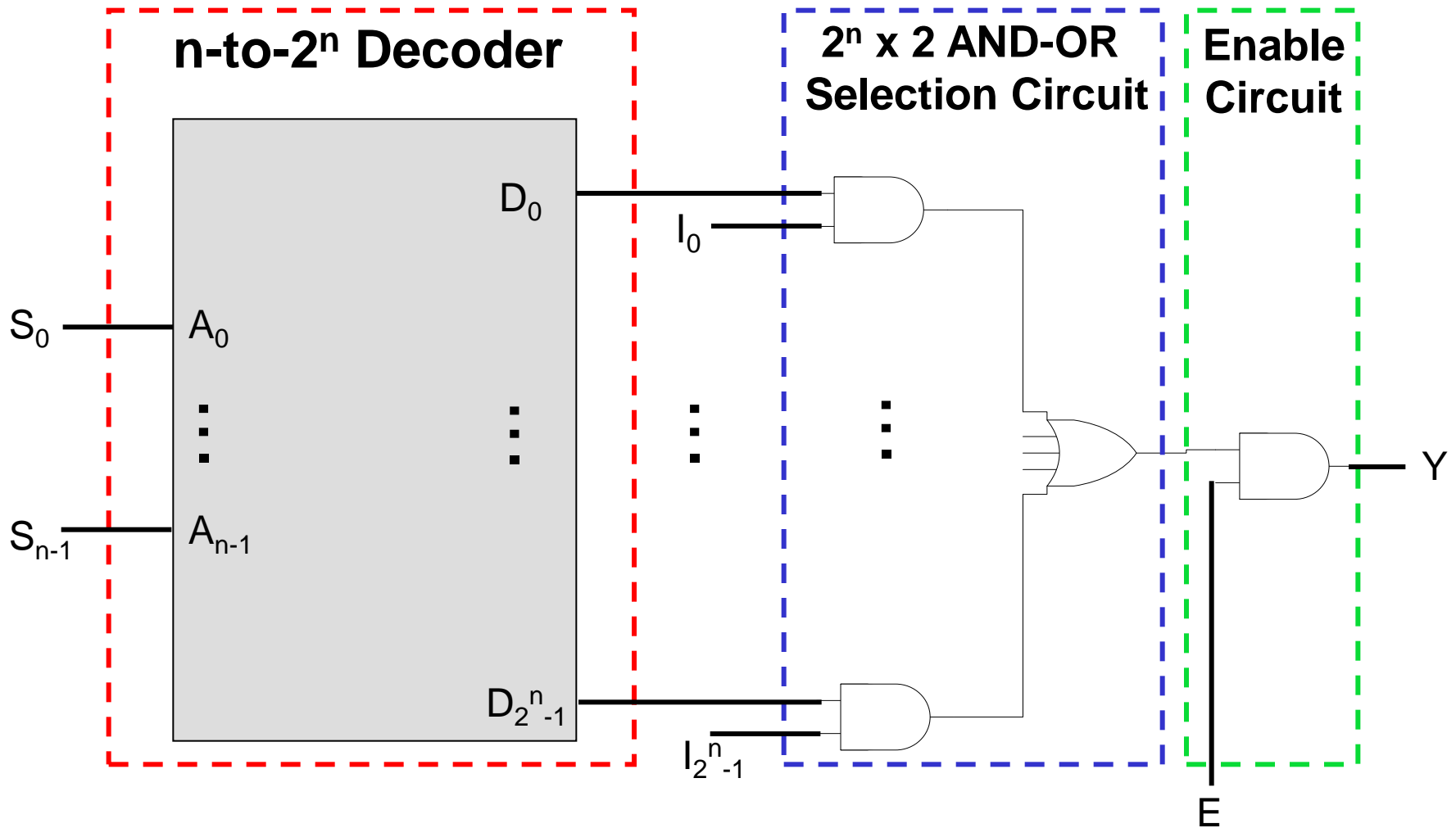

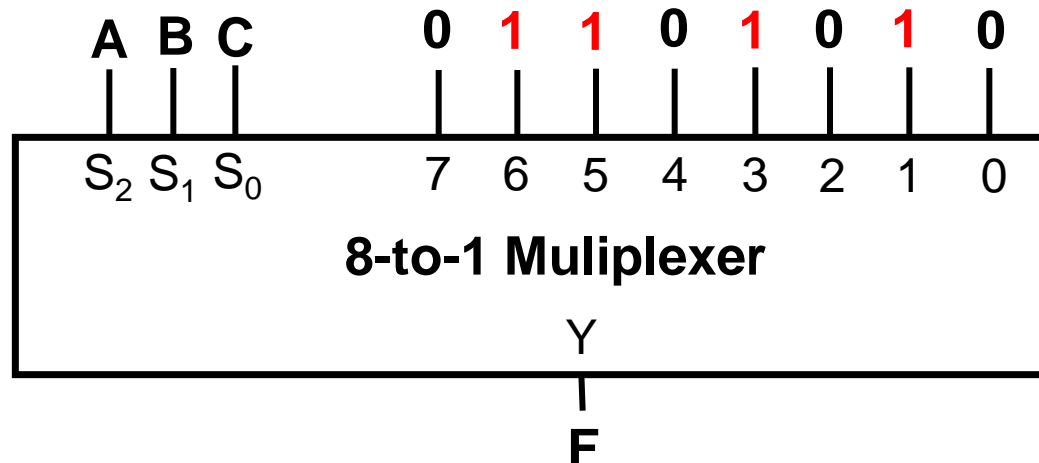
# Implementing Boolean Functions using Multiplexers

- Any Boolean function of  $n$  variables can be implemented using a  $2^n$ -to-1 Multiplexer. Why?
  - Multiplexer is **basically a decoder with outputs ORed together!**
  - SELECT signals generate the minterms of the function
  - The data inputs identify which minterms are to be combined with an OR
- Example: Consider function  $F(A,B,C) = \sum m(1,3,5,6)$ 
  - It has 3 variables, therefore we can implement it with 8-to-1 MUX


 
# Another Example

- Consider function  $F(A,B,C,D)$  specified by the truth table on the right-hand side
- $F$  has 4 variables  $\rightarrow$  we use 16-to-1 MUX



A	B	C	D	F
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1


# Efficient Method for Implementing Boolean Functions using Multiplexers

- We have seen that implementing a function of  $n$  variables with  $2^n$ -to-1 MUX is straightforward.
- However, there exist **more efficient method** where any function of  $n$  variables can be implemented with  **$2^{n-1}$ -to-1** MUX. Consider an arbitrary function  $F(X_1, X_2, \dots, X_n)$ :
  - We need a  **$2^{n-1}$**  line MUX with  **$n-1$**  select lines.
  - Enumerate function as a truth table with consistent ordering of variables, i.e.,  **$X_1, X_2, \dots, X_n$** .
  - Attach the **most significant  $n-1$**  variables to the  **$n-1$**  select lines, i.e.,  **$X_1, X_2, \dots, X_{n-1}$**
  - Examine pairs of adjacent rows. The **least significant variable** in each pair is  **$X_n = 0$**  and  **$X_n = 1$** .
  - Determine whether the function output **F** for the  $(X_1, X_2, \dots, X_{n-1}, 0)$  and  $(X_1, X_2, \dots, X_{n-1}, 1)$  combination is  $(0,0)$ ,  $(0,1)$ ,  $(1,0)$ , or  $(1,1)$ .
  - Attach  $0$ ,  $X_n$ ,  $X_n'$ , or  $1$  to the data input corresponding to  $(X_1, X_2, \dots, X_{n-1})$  respectively.

# Example

- Again, consider function  $F(A,B,C) = \sum m(1,3,5,6)$
- It has 3 variables
- We can implement it using **4-to-1 MUX** instead of 8-to-1 MUX.

A	B	C	F	
0	0	0	0	<b>F = C</b>
0	0	1	1	
0	1	0	0	<b>F = C</b>
0	1	1	1	
1	0	0	0	<b>F = C</b>
1	0	1	1	
1	1	0	1	<b>F = C'</b>
1	1	1	0	

 




# Another Example


- Again, consider function  $F(A,B,C,D)$  specified by the truth table below.  $F$  has 4 variables  $\rightarrow$  we use 8-to-1 MUX instead of 16-to-1 MUX.

A	B	C	D	F	
0	0	0	0	0	$F = D$
0	0	0	1	1	
0	0	1	0	0	$F = D$
0	0	1	1	1	
0	1	0	0	1	$F = \bar{D}$
0	1	0	1	0	
0	1	1	0	0	$F = 0$
0	1	1	1	0	
1	0	0	0	0	$F = 0$
1	0	0	1	0	
1	0	1	0	0	$F = D$
1	0	1	1	1	
1	1	0	0	1	$F = 1$
1	1	0	1	1	
1	1	1	0	1	$F = 1$
1	1	1	1	1	

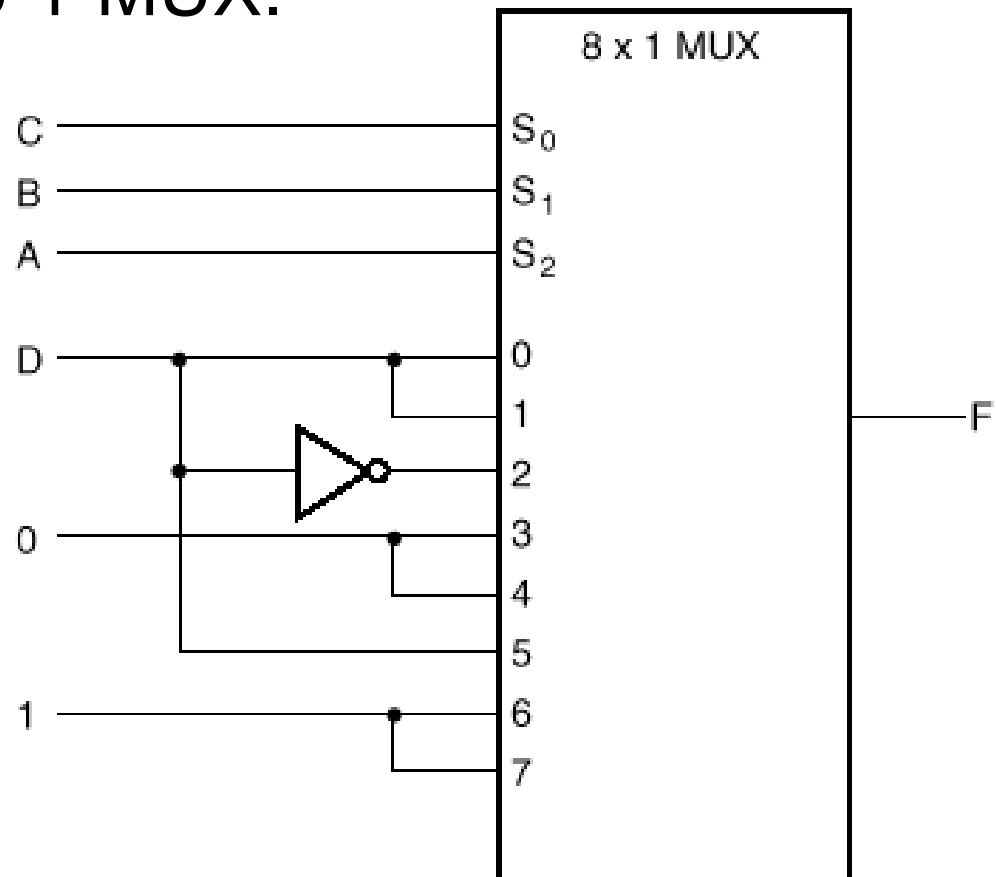

 
# MUX as a Universal Gate


- We can construct **OR**, **AND**, and **NOT** gates using **2-to-1 MUX**
- Thus, **2-to-1 MUX** is a universal gate!
- Recall the equation of 2-to-1 MUX:  **$Z = S \cdot I_1 + S' \cdot I_0$**


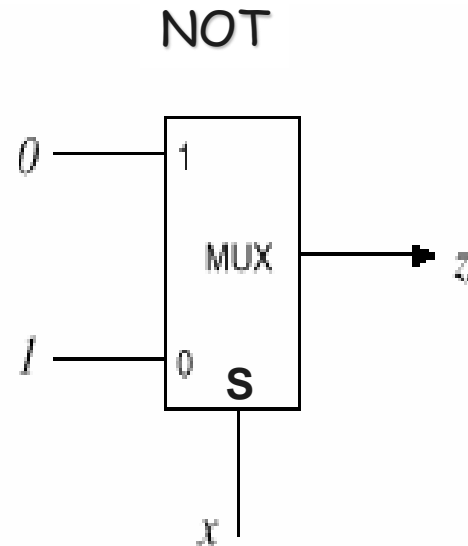
$$\begin{aligned} z &= x_1 \cdot 1 + x_1' \cdot x_0 \\ &= x_1 + x_1' \cdot x_0 \\ &= (x_1 + x_1') \cdot (x_1 + x_0) \\ &= 1 \cdot (x_1 + x_0) = x_1 + x_0 \end{aligned}$$



 
$$\begin{aligned} z &= x \cdot 0 + x' \cdot 1 \\ &= x' \end{aligned}$$



$$\begin{aligned} z &= x_0 \cdot x_1 + x_0' \cdot 0 \\ &= x_0 \cdot x_1 \end{aligned}$$

 
# Multiplexer Expansions

- **Larger** multiplexers can be constructed using a number of smaller ones
- Use **composition** of smaller multiplexers
- Example:
  - Given: 4-to-1 multiplexers
  - Required: 8-to-1 multiplexer
  - Solution: Each multiplexer selects half of the data inputs. Enable signal selects which multiplexer is active:
    - $S_2 = 0$ : enable top multiplexer
    - $S_2 = 1$ : enable bottom multiplexer



 
# Multiplexer Expansions (cont.)

- Until now, we have examined 1-bit data inputs selected by a MUX



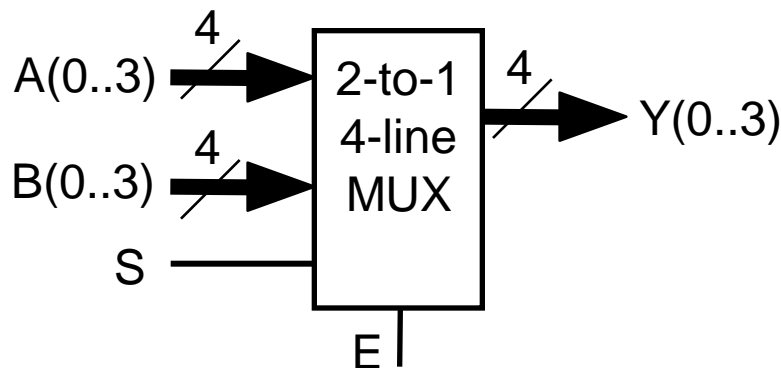- What if we want to select **m-bit** data/words?
  - Example: MUX that selects between 2 sets of 4-bit inputs



E	S	Y(0..3)
1	0	A(0..3)
1	1	B(0..3)
0	x	0000

- How to construct this 2-to-1 4-line MUX?

# Example: 2-to-1 4-line Multiplexer

- Uses four 2-to-1 MUXs with common select (S) and enable (E)
- Select line chooses between  $A_i$ 's and  $B_i$ 's. The selected four-wire digital signal is sent to the  $Y_i$ 's
- Enable line turns MUX on and off ( $E=1$  is on)

