



# Sequential Circuits: Basic Concept

---




# Overview

---

- Sequential Circuits
  - Sequential vs. Combinational Circuits
- Types of Sequential Circuits
  - Synchronous vs. Asynchronous Circuits
- Sequential Circuit Representations
  - Boolean Equations
    - Characteristic (Flip-Flop Input) Equations
    - Primary Output Equations
  - State Table
  - State Diagram
- Finite State Machines
  - Mealy vs. Moore Machines
 
# Combinational vs. Sequential Circuits


- Combinational circuits are **memory-less** and **do not have feed-back loops**. Thus, the output values depend **ONLY** on the current input values.



- Able to perform useful operations (add, subtract, multiply, encode, decode, multiplex, demultiplex, etc...).
- However, the performance of useful sequences of operations using only combinational circuits requires cascading many structures together.
- Thus, the hardware to do this is **very costly** and **inflexible**.
- To perform useful or flexible sequences of operations, we need to construct circuits that can **store** information between the operations.
- Such circuits are called **Sequential Circuits**.
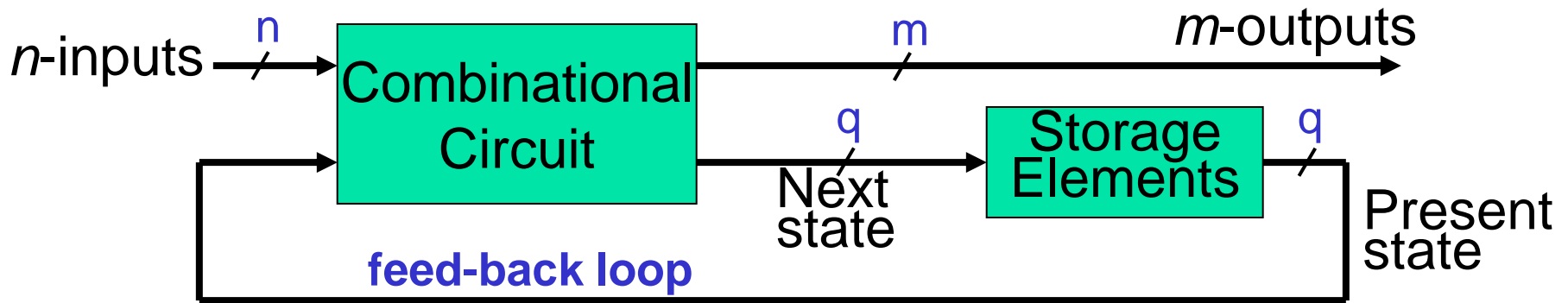
# Sequential Circuits

- Sequential circuits consist of **combinational logic** as well as **memory elements** (used to store certain circuit states). Outputs depend on **BOTH** current input values and previous input values (kept in the storage elements).



- There is a **feed-back loop** in the sequential circuits.
- The storage elements are circuits that are capable of storing binary information.
- One storage element can store one bit of information.


# Storage Elements

- Two types of storage elements are used in Sequential Circuits: **Latches** and **Flip-Flops**.

- Latches (D, SR, JK, T)**

- General description of a latch:

 
- 1-bit storage device with several inputs ( $X$ ) and an output ( $Q$ ).
- Output is changed  $Q = f(X)$  only when **specific combinations** occur at the inputs  $X$ ; otherwise the output remains unchanged (storage mode).



- Flip-Flops (D, SR, JK, T)**

- General description of a Flip-Flop:

 - 1-bit storage device with several inputs ( $X$ ), an output ( $Q$ ), and a specific **trigger** input ( $CLK$ ).
- Output is changed  $Q = f(X)$  on **response of a pulse at the trigger input  $CLK$**  (on the **rising** or **falling** edge of the pulse). When a pulse is absent at input  $CLK$  the output remains unchanged (storage mode).



- More details about Latches and Flip-Flops later!**




# Types of Sequential Circuits

---


- Sequential circuits are divided into two main types depending on the storage elements that are used in the feed-back loop.
- **Synchronous** Sequential Circuits
  - Circuits with Flip-Flops in the feedback loop
- **Asynchronous** Sequential Circuits
  - Circuits without storage elements in the feed-back loop  
OR
  - Circuits with Latches in the feed-back loop
- We will not study asynchronous circuits
  - Only brief description and comparison will follow.

# Asynchronous Sequential Circuits

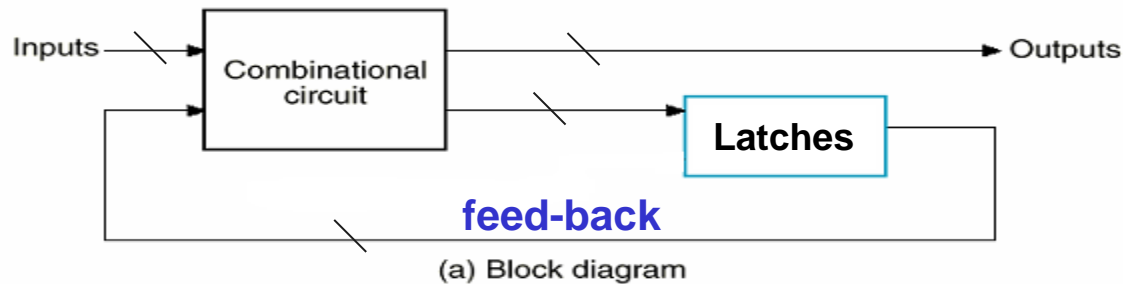

- The behavior is dependent on the order of input signal changes over continuous time, and output can change at **any** time (**clockless**).
- The Latches receive their inputs from the combinational circuit.
- The Latches can change state **as soon as their inputs are changed**.
  - Thus, a transition from one state to the other may occur at **any** time.
  - This makes the design and analysis of the circuit **very difficult**.
- If a circuit is not designed properly its behavior may become unpredictable:
  - The new state may change the Latches again through the **feed-back loop**.
  - This may lead to a **succession of changes of state** instead of a single change even if we do not change the inputs of the circuit:
    - The circuit comes to a stable state after several state transitions.
    - The transition from one state to another may never stop.

# Synchronous Sequential Circuits

 

$T$  – clock period

$1/T$  – clock frequency

$W/T$  – duty cycle

(a) Block diagram



rising edge  
falling edge

(b) Timing diagram of clock pulses

- The behavior can be defined from knowledge of its signals at discrete instants of time.
  - Circuit achieves synchronization by using a timing signal called the **clock**
- The Flip-Flops receive their inputs from the combinational circuit.
- The Flip-Flops can change state only in response to a **clock pulse** on **rising** or **falling** edge.
- When a clock pulse is absent the Flip-Flop outputs cannot change even if the combinational circuit driving the flip-flop inputs changes in value.
- Thus, a transition from one state to the other occurs **only at fixed time intervals** dictated by the clock pulse, giving synchronous operation.



# Synchronous vs. Asynchronous Sequential Circuits

## ■ Storage Elements:

- In synchronous sequential circuits - **FLIP-FLOPs**.
- In asynchronous sequential circuits - either **Latches** or **gate circuits** with feedback producing the effect of latch operation.

## ■ State Changes:

- In a synchronous sequential circuit a change of state occurs **only in response to a synchronizing clock pulse**. All the FLIP-FLOPs are clocked **simultaneously** by a common clock pulse.
- In an asynchronous sequential circuit, the state of the circuit can change **immediately when an input change occurs**. It does not use a clock.

## ■ Circuit Speed:

- In synchronous sequential circuits, the speed of operation depends on the **maximum allowed clock frequency**
  - because states are changed only on response of a clock pulse.
- Asynchronous sequential circuits do not require clock pulses and they can change state with the input change.
  - Therefore, in general the asynchronous sequential circuits are **faster** than the synchronous sequential circuits.

# Synchronous vs. Asynchronous Sequential Circuits (cont.)

## ■ Input Changes:

- In synchronous sequential circuits input changes are assumed to **occur between clock pulses**. The circuit must be in the stable state before next clock pulse arrives.
- In asynchronous sequential circuits input changes should occur **only when the circuit is in a stable state**.

## ■ Number of Inputs that can Change:

- In synchronous sequential circuits, **any number** of inputs can change **simultaneously** (during the absence of the clock).
- In asynchronous sequential circuits **only one** input is allowed to change at a time. If more than one inputs change simultaneously, the circuit makes erroneous state transitions due to different delay paths for each input variable.

## ■ Output Changes


- In synchronous sequential circuits outputs change at **any time** when inputs change or **on response to a clock pulse**.
- In asynchronous sequential circuits outputs change at **any time** when inputs are changed.

# Synchronous vs. Asynchronous Sequential Circuits (cont.)

- Nowadays, most of the sequential circuits are **synchronous** due to
  - their **predictability** and
  - relatively **easy design and analysis**.
- An **asynchronous circuit** is preferred over synchronous circuit when **high speed of operations are required**
  - asynchronous circuits respond immediately without having to wait for a clock pulse.
- **Asynchronous** sequential circuits **cost less** in terms of number of gates than the synchronous circuits
  - therefore, for economical reasons, they find useful applications.

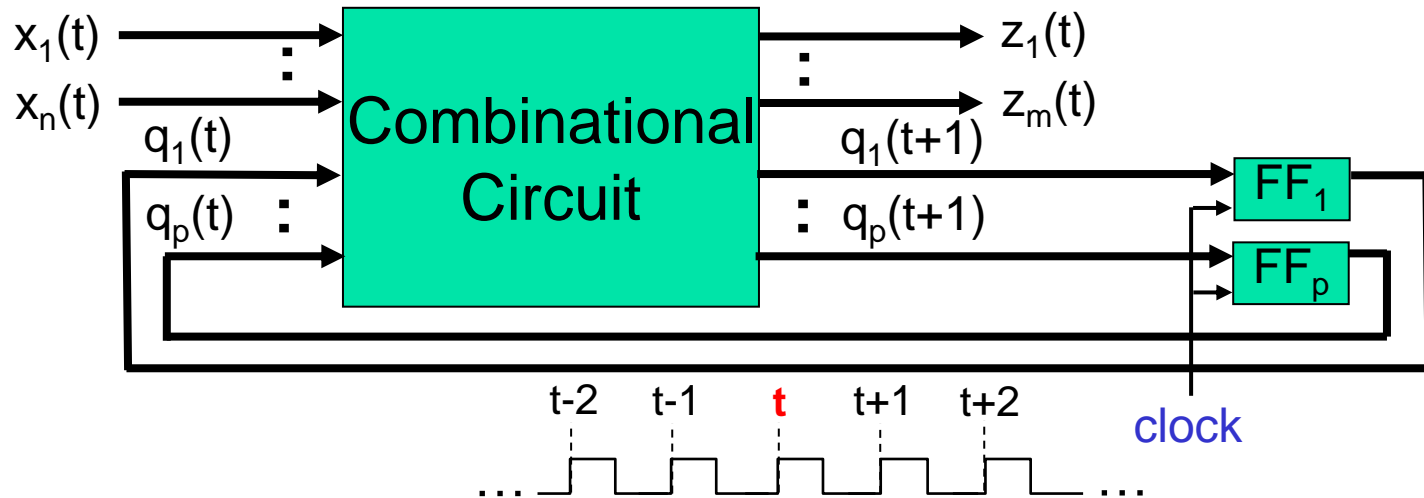
# Synchronous Sequential Circuits: Definitions and Notations

- Consider the sequential circuit below which has  $n$  inputs,  $m$  outputs, and  $p$  Flip-Flops (storage elements):



- $x_j(t)$  – the **present value** of input  $x_j$ , i.e., the value prior to the application of a clock pulse at time  $t$ .
- $z_j(t)$  – the **present value** of output  $z_j$ , i.e., the value prior to the application of a clock pulse at time  $t$ .
- $q_j(t)$  – the **present value** stored by  $FF_j$ , i.e., the value prior to the application of a clock pulse at time  $t$ .
- $q_j(t+1)$  – the **next value** to be stored by  $FF_j$ , i.e., the value stored after the application of a clock pulse at time  $t$ .
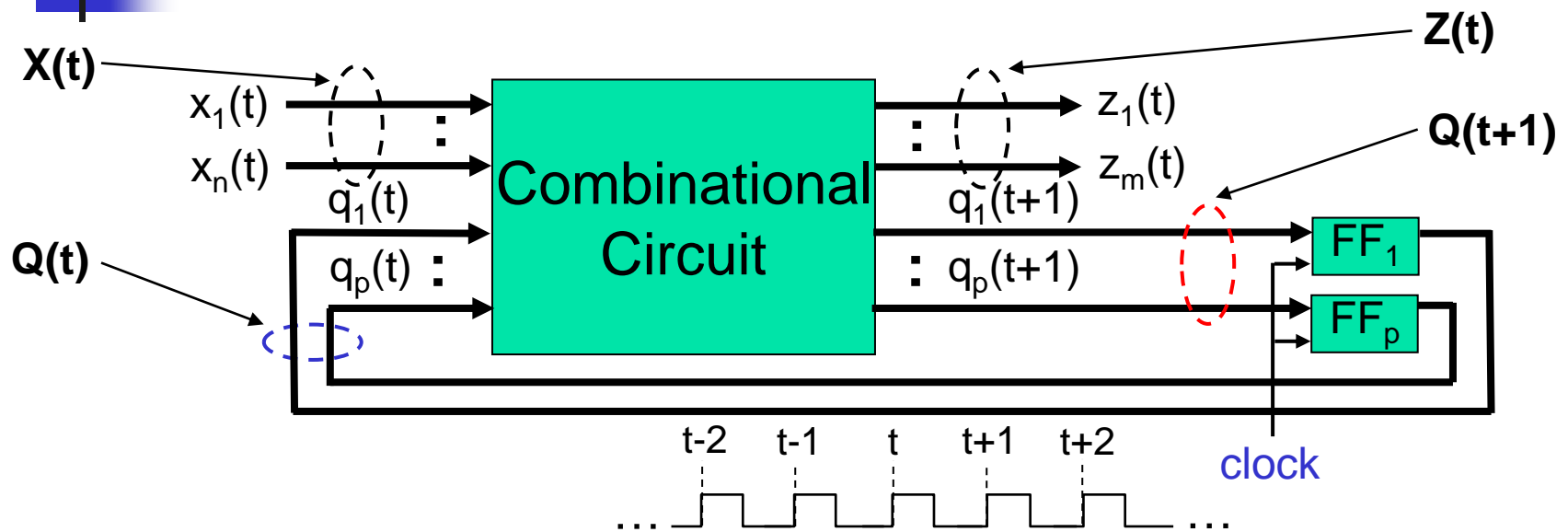
# Synchronous Sequential Circuits: Definitions and Notations (cont.)



- **Input Vector**  $X(t) = (x_1(t), \dots, x_n(t))$  – the values at the inputs prior to the application of a clock pulse at time  $t$ .
- **Output Vector**  $Z(t) = (z_1(t), \dots, z_m(t))$  – the values at the outputs prior to the application of a clock pulse at time  $t$ .
- **Present State**  $Q(t) = (q_1(t), \dots, q_p(t))$  – the values stored by the Flip-Flops prior to the application of a clock pulse at time  $t$ .
- **Next State**  $Q(t+1) = (q_1(t+1), \dots, q_p(t+1))$  – the values stored by the Flip-Flops after the application of a clock pulse at time  $t$ . In other words, **the state one clock period later**.




# Sequential Circuit Representations

---

- Boolean Equations
  - Characteristic (Flip-Flop Input) Equations
  - Primary Output Equations
- State Table
- State Diagram

# Characteristic (FF Input) Equations

 


- An algebraic representation used to fully specify the combinational logic that drives the inputs of the FFs.
- Set of Boolean Equations:  

$$q_1(t+1) = f_1( x_1(t), \dots, x_n(t), q_1(t), \dots, q_p(t) )$$

$$\vdots$$

$$q_p(t+1) = f_p( x_1(t), \dots, x_n(t), q_1(t), \dots, q_p(t) )$$
- Short Notation:  $Q(t+1) = F( X(t), Q(t) )$
- The next state  $Q(t+1)$  depends on the present state  $Q(t)$  and the input vector  $X(t)$ .

# Primary Output Equations


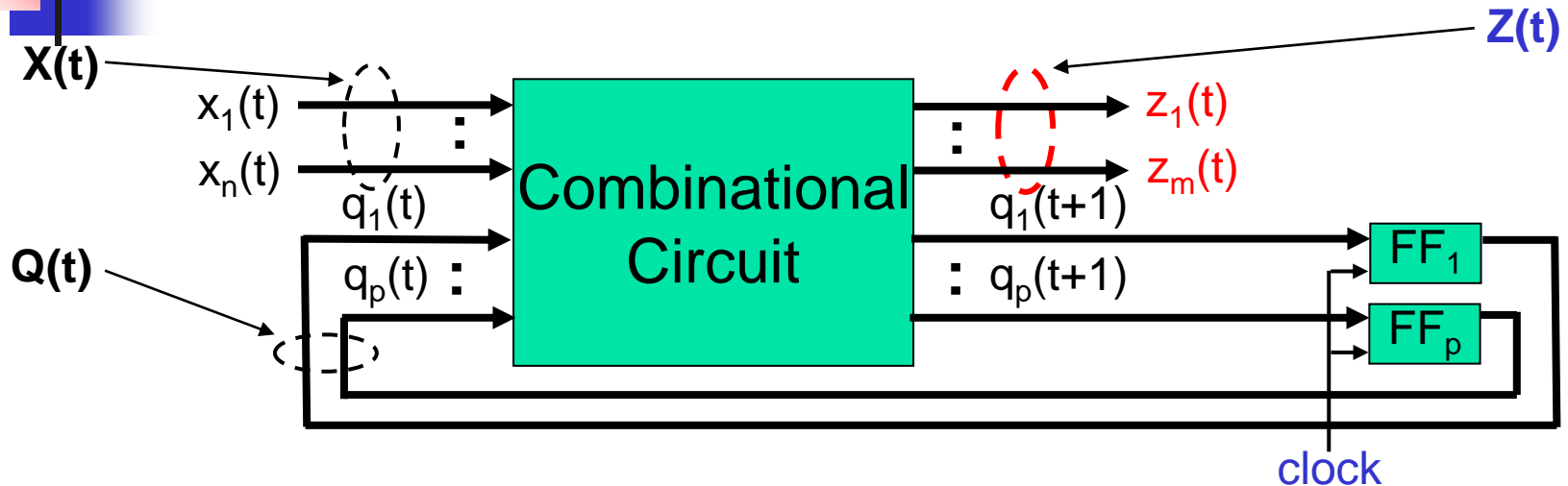


- An algebraic representation used to fully specify the combinational logic that defines the outputs of the circuit.
- Set of Boolean Equations:  
$$z_1(t) = g_1(x_1(t), \dots, x_n(t), q_1(t), \dots, q_p(t))$$
$$\vdots$$
$$z_m(t) = g_m(x_1(t), \dots, x_n(t), q_1(t), \dots, q_p(t))$$
- Short Notation:  $Z(t) = G(X(t), Q(t))$
- The output vector  $Z(t)$  depends on the present state  $Q(t)$  and the input vector  $X(t)$ .



 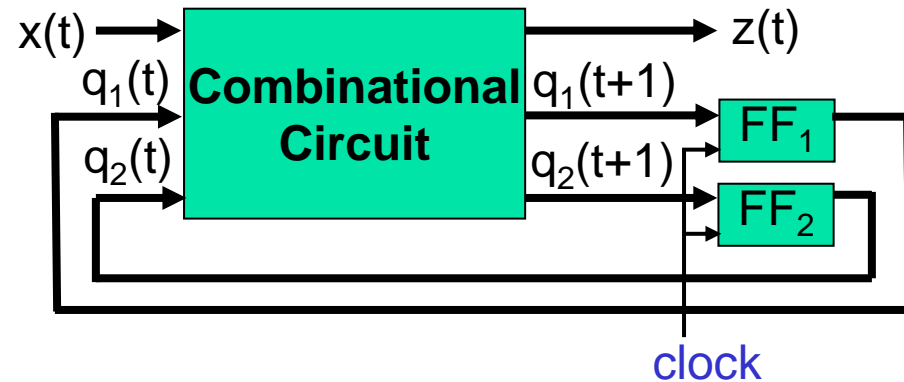
# Example: Equations

- Consider simple sequential circuit:
  - 1 input , 1 output , 2 Flip-Flops
- Characteristic (FF input) equations:
  - $q_1(t+1) = f_1( x(t), q_1(t), q_2(t) )$   
 $= q_1(t) \cdot x(t) + q_2(t) \cdot x(t)$   
 $= ( q_1(t) + q_2(t) ) \cdot x(t)$
  - $q_2(t+1) = f_2( x(t), q_1(t), q_2(t) )$   
 $= q_1(t)' \cdot x(t)$
- Primary output equations:
  - $z(t) = g( x(t), q_1(t), q_2(t) )$   
 $= q_1(t) \cdot x(t)' + q_2(t) \cdot x(t)$   
 $= ( q_1(t) + q_2(t) ) \cdot x(t)'$


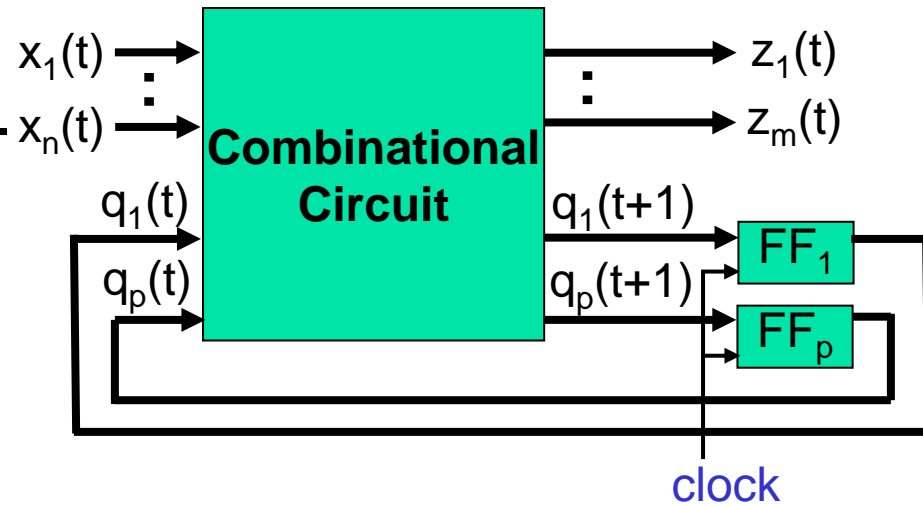
# State Table

- Enumerates the relationship between inputs, outputs, and states of the sequential circuit.
- Given a circuit with  $n$  inputs,  $m$  outputs, and  $p$  Flip-Flops:
  - The corresponding state table contains  $2^{n+p}$  rows.
  - The corresponding state table contains  $n+2p+m$  columns.



Inputs			Present State			Next State			Outputs		
$x_1(t)$	...	$x_n(t)$	$q_1(t)$	...	$q_p(t)$	$q_1(t+1)$	...	$q_p(t+1)$	$z_1(t)$	...	$x_m(t)$
0	...	0	0	...	0						
0	...	0	0	...	1						
...											
1	...	1	1	...	0						
1	...	1	1	...	1						

$n+p+p+m$


# Example: State Table

- Consider previous example:
  - 1 input , 1 output , 2 Flip-Flops
- Equations:

$$q_1(t+1) = x(t) \cdot q_2(t) + x(t) \cdot q_1(t)$$

$$q_2(t+1) = x(t) \cdot q_1(t)'$$
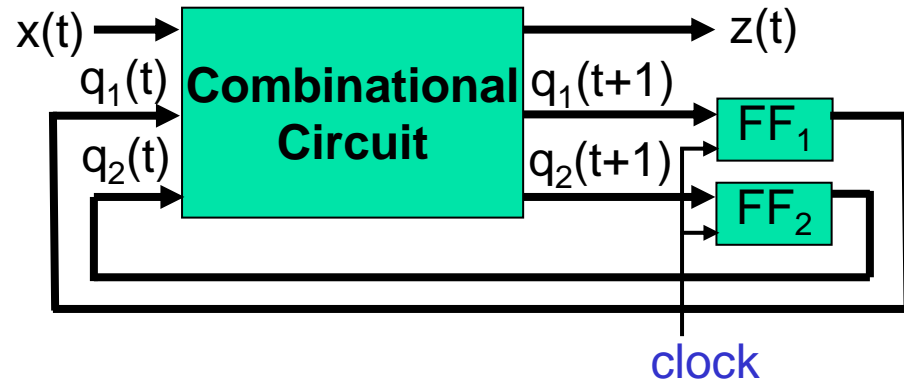
$$z(t) = x(t)' \cdot q_2(t) + x(t) \cdot q_1(t)$$



## State Table

- $2^2 = 4$  states
  - Q1 = 00
  - Q2 = 01
  - Q3 = 10
  - Q4 = 11
- How do you read this table?

Inputs	Present State		Next State		Outputs
	x(t)	q <sub>1</sub> (t)	q <sub>2</sub> (t)	q <sub>1</sub> (t+1)	
0	0	0	0	0	0
0	0	1	0	0	1
0	1	0	0	0	1
0	1	1	0	0	1
1	0	0	0	1	0
1	0	1	1	1	0
1	1	0	1	0	0
1	1	1	1	0	0

# State Table to/from Equations

## ■ State Table to Equations

- Treat the State Table as a Truth Table of Boolean functions to get the Characteristic and Primary Output Equations.
- You can derive the CSOP or CPOS form of the Equations directly using the **right part** of the State Table.
- You can simplify the Equations using algebraic manipulations or K-maps.

Inputs			Present State			Next State			Outputs		
$x_1(t)$	...	$x_n(t)$	$q_1(t)$	...	$q_p(t)$	$q_1(t+1)$	...	$q_p(t+1)$	$z_1(t)$	...	$x_m(t)$
0	...	0	0	...	0						
0	...	0	0	...	1						
...											
1	...	1	1	...	0						
1	...	1	1	...	1						

right part of the table

## ■ State Table from Equations

- The Characteristic and Primary Output Equations are Boolean functions.
- Represent the Equations in a common Truth Table. This is actually the State Table.

# Example: State Table to Equations

Inputs $x(t)$	Present State		Next State		Outputs $z(t)$
	$q_1(t)$	$q_2(t)$	$q_1(t+1)$	$q_2(t+1)$	
0	0	0	0	0	0
0	0	1	0	0	1
0	1	0	0	0	1
0	1	1	0	0	1
1	0	0	0	1	0
1	0	1	1	1	0
1	1	0	1	0	0
1	1	1	1	0	0

## Equations in CSOP form

$$q_1(t+1) = x(t) \cdot q_1(t)' \cdot q_2(t) + x(t) \cdot q_1(t) \cdot q_2(t)' + x(t) \cdot q_1(t) \cdot q_2(t)$$

$$q_2(t+1) = x(t) \cdot q_1(t)' \cdot q_2(t)' + x(t) \cdot q_1(t)' \cdot q_2(t)$$

$$z(t) = x(t)' \cdot q_1(t)' \cdot q_2(t) + x(t)' \cdot q_1(t) \cdot q_2(t)' + x(t) \cdot q_1(t) \cdot q_2(t)$$

Simplified Equations



		$q_1 q_0$			
		00	01	11	10
$x$	0				
	1		1	1	1
		$q_2$			

$$q_1(t+1) = x(t) \cdot q_2(t) + x(t) \cdot q_1(t)$$

		$q_1 q_0$			
		00	01	11	10
$x$	0				
	1	1	1		
		$q_2$			


$$q_2(t+1) = x(t) \cdot q_1(t)'$$

		$q_1 q_0$			
		00	01	11	10
$x$	0				
	1		1	1	1
		$q_2$			

$$z(t) = x(t)' \cdot q_2(t) + x(t)' \cdot q_1(t)$$
 
# Example: State Table from Equations

$$q_1(t+1) = x(t) \cdot q_2(t) + x(t) \cdot q_1(t)$$
$$q_2(t+1) = x(t) \cdot q_1(t)'$$
$$z(t) = x(t)' \cdot q_2(t) + x(t)' \cdot q_1(t)$$



Follow the procedure described below


Inputs	Present State		Next State		Outputs
x(t)	q <sub>1</sub> (t)	q <sub>2</sub> (t)	q <sub>1</sub> (t+1)	q <sub>2</sub> (t+1)	z(t)
0	0	0	0	0	0
0	0	1	0	0	1
0	1	0	0	0	1
0	1	1	0	0	1
1	0	0	0	1	0
1	0	1	1	1	0
1	1	0	1	0	0
1	1	1	1	0	0

- Identify the variables that are used on the right-hand side of the equations
  - x(t), q<sub>1</sub>(t), and q<sub>2</sub>(t) → 3 variables
- List all possible combinations of the above variables:
  - 2<sup>3</sup> = 8 combinations
- For each combination evaluate the Equations:
  - Find the value of q<sub>1</sub>(t+1), q<sub>2</sub>(t+1), and z(t)

# State Diagram

- Graph representation of a state table.



Inputs			Present State			Next State			Outputs		
$x_1(t)$	...	$x_n(t)$	$q_1(t)$	...	$q_p(t)$	$q_1(t+1)$	...	$q_p(t+1)$	$z_1(t)$	...	$x_m(t)$
0	...	0	0	...	0						
0	...	0	0	...	1						
1	...	1	1	...	0						
1	...	1	1	...	1						

 


- Graph **node** with label **Q** denotes state **Q**.
- Graph **edge** with label **X** denotes transition between two states when input **X** is applied.
- The graph has  **$2^p$  nodes** and  **$2^{n+p}$  edges**. Why?
  
# Example: State Diagram

- Possible states = { 00, 01, 10, 11 }  
→ 4 nodes in the diagram
- Possible Transitions = #rows in table  
→ 8 edges in the diagram



Inputs x(t)	Present State		Next State		Outputs z(t)
	q <sub>1</sub> (t)	q <sub>2</sub> (t)	q <sub>1</sub> (t+1)	q <sub>2</sub> (t+1)	
0	0	0	0	0	0
0	0	1	0	0	1
0	1	0	0	0	1
0	1	1	0	0	1
1	0	0	0	1	0
1	0	1	1	1	0
1	1	0	1	0	0
1	1	1	1	0	0

 

Reads as:

When at state **Q1** and apply vector **X**, we get output **Z** and proceed to state **Q2**.






# Finite State Machines

---

- The synchronous sequential circuits also can be called **Finite State Machines (FSM)**. Why?
- A sequential circuit with  $p$  Flip-Flops
  - can have  $2^p$  distinct states.
  - can have  $2^p \times 2^p = 2^{2p}$  distinct transitions.
- So, it has **finite** number of distinct states and transitions, hence the name.
- FSM is also one of the so called **Models of Computation**.
- There are two types of FSM:
  - **Mealy** model FSM
  - **Moore** model FSM

# Mealy Finite State Machine

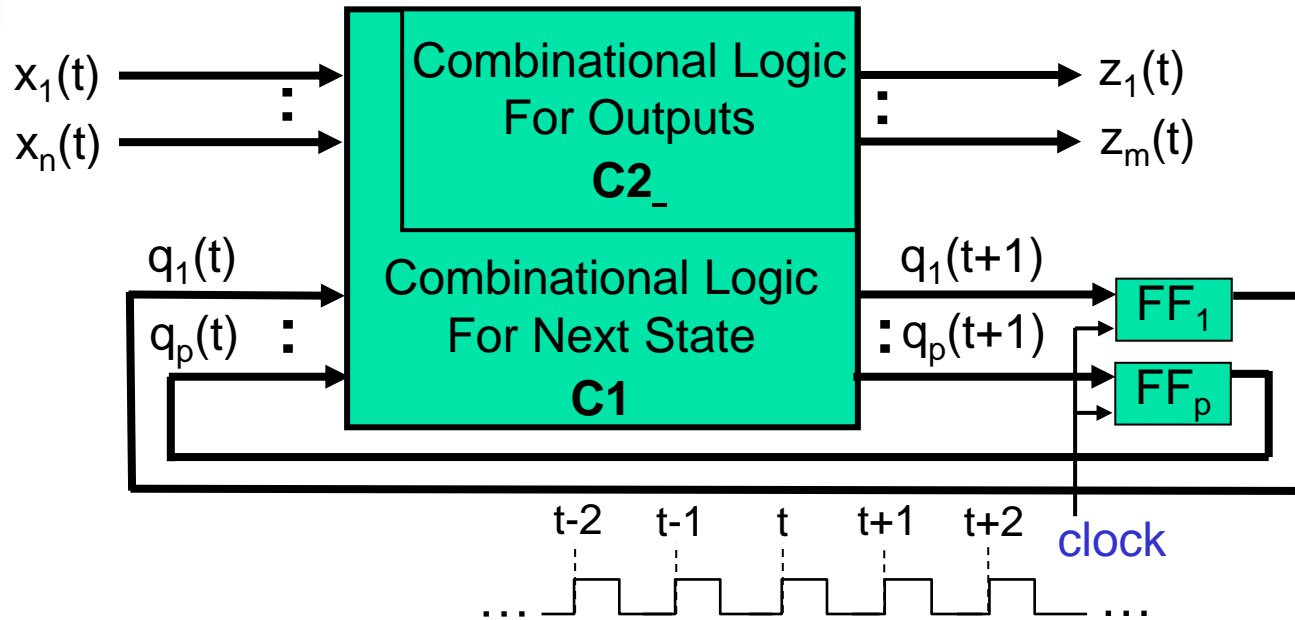

- Both outputs and next state depend directly on both primary inputs **AND** present state.



$$Q(t+1) = C1( X(t), Q(t) )$$

$$Z(t) = C2( X(t), Q(t) )$$

- Outputs are **asynchronous**, i.e., they can change in response to any changes in the inputs, **independent** of the clock.
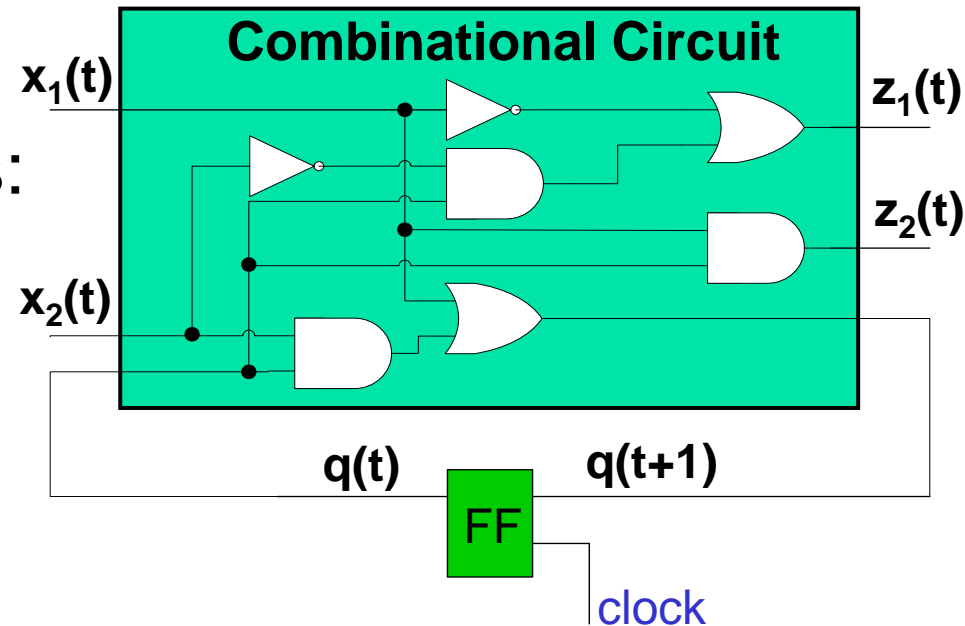 
# Example: Mealy Machine




- Consider simple sequential circuit:
  - 2 input , 2 output , 1 Flip-Flop
- Characteristic (FF input) equations:
  - $q(t+1) = x_1(t) + x_2(t) \cdot q(t)$
- Primary output equations:
  - $z_1(t) = x_1(t)' + x_2(t)' \cdot q(t)$
  - $z_2(t) = x_1(t) \cdot q(t)$




# Example: Mealy Machine (cont.)

- Possible states =  $\{0,1\}$ , thus 2 nodes in state diagram
- Possible Transitions = #rows in the table, thus 8 edges in state diagram

Inputs		PS		NS	Outputs	
$x_1(t)$	$x_2(t)$	$q(t)$		$q(t+1)$	$z_1(t)$	$z_2(t)$
0	0	0		0	1	0
0	0	1		0	1	0
0	1	0		0	1	0
0	1	1		1	1	0
1	0	0		1	0	0
1	0	1		1	1	1
1	1	0		1	0	0
1	1	1		1	0	1

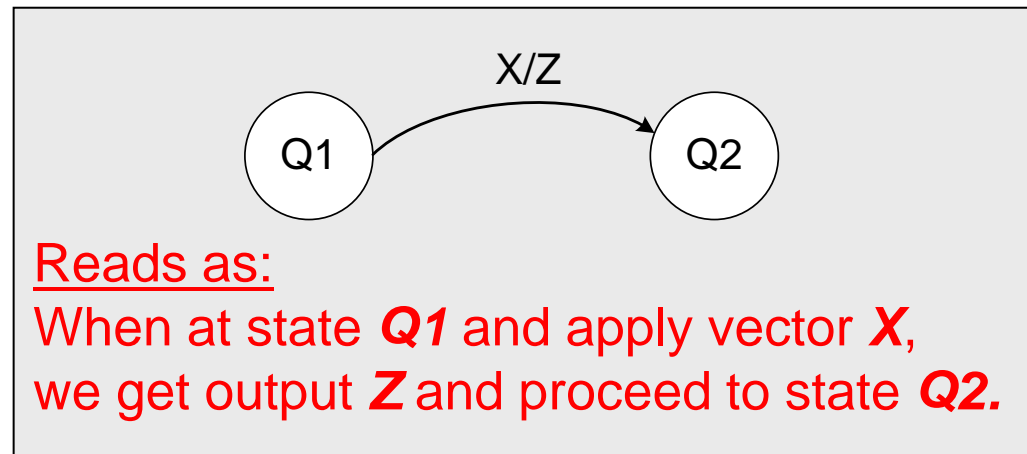  

# Moore Finite State Machine

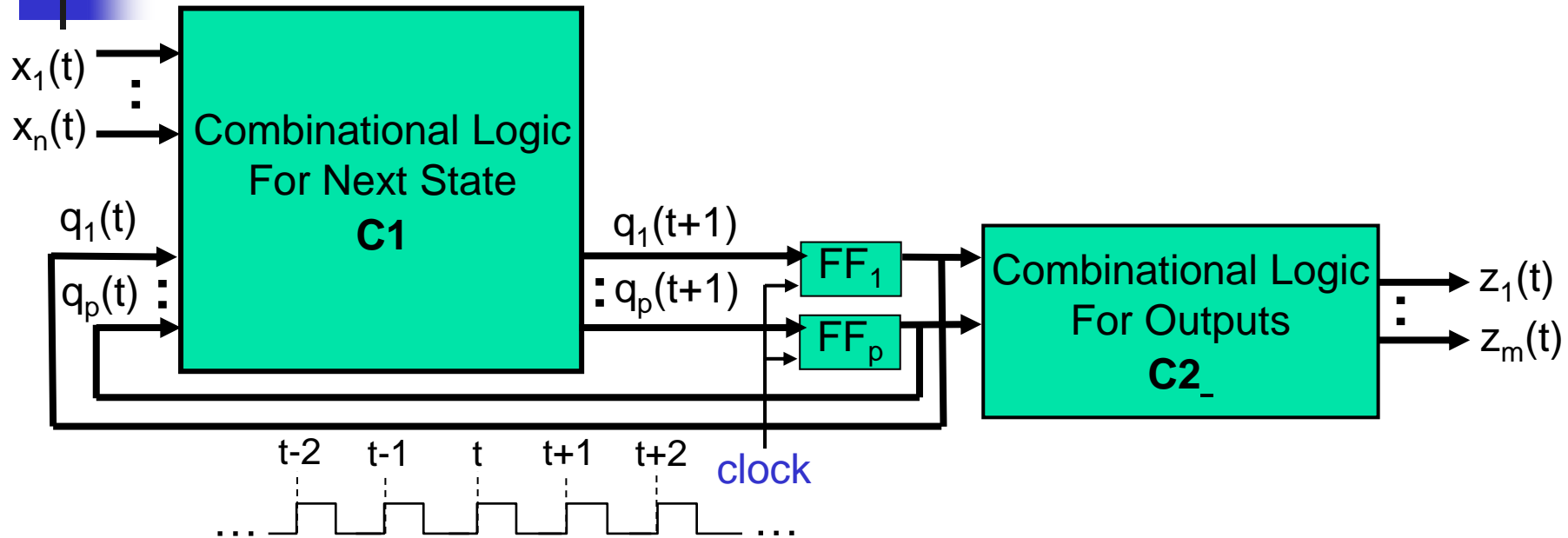

- Next state depends directly on both primary inputs **AND** present state. Outputs depend directly **only** on present state.



$$Q(t+1) = C1( X(t), Q(t) )$$

$$Z(t) = C2( Q(t) ) = C2( C1( X(t-1), Q(t-1) ) )$$

- Moore outputs are **synchronous** with the clock, only changing with state transitions.
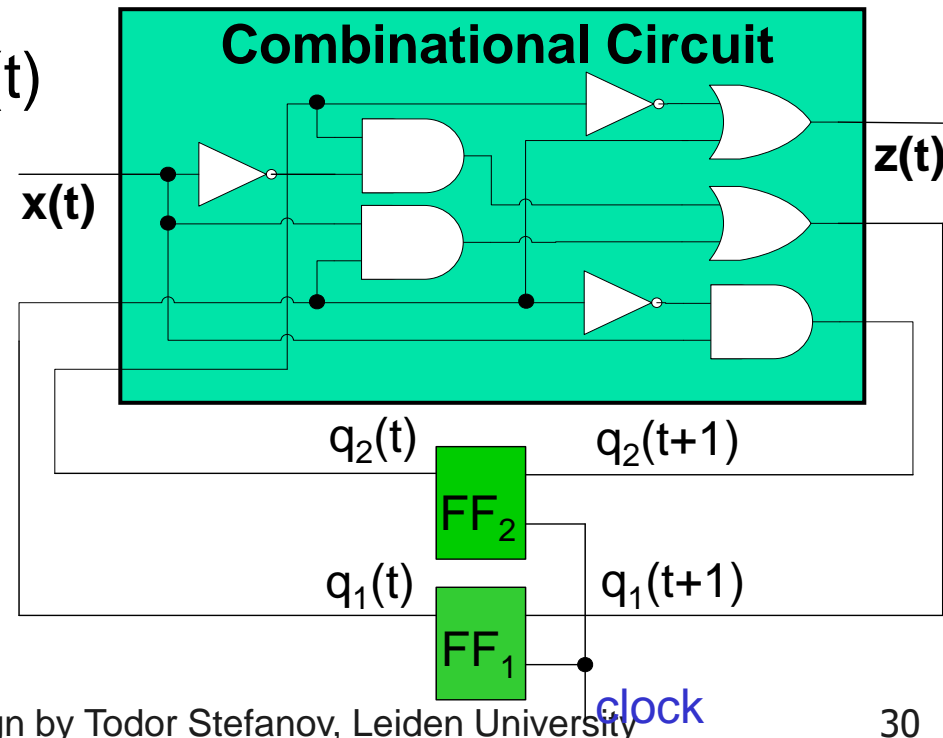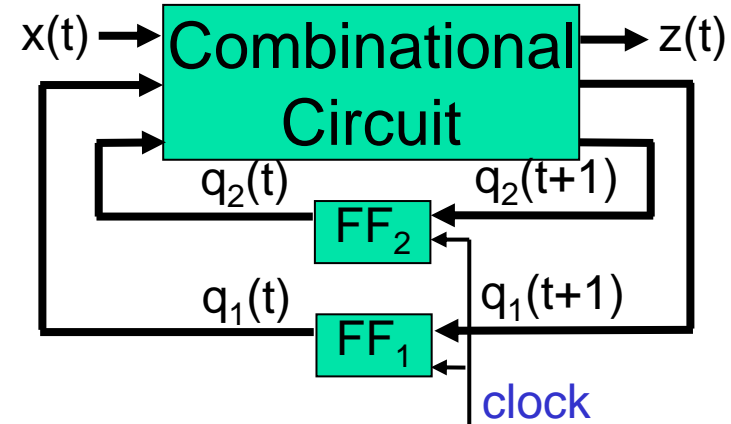
# Example: Moore Machine



- Consider simple sequential circuit:
  - 1 input , 1 output , 2 Flip-Flops
- Characteristic (FF input) equations:
  - $q_1(t+1) = x(t) \cdot q_1(t) + x(t)' \cdot q_2(t)$
  - $q_2(t+1) = x(t) \cdot q_1(t)'$
- Primary output equations:
  - $z(t) = q_1(t) + q_2(t)'$



# Example: Moore Machine (cont.)

Inputs x(t)	Present State		Next State		Outputs z(t)
	q <sub>1</sub> (t)	q <sub>2</sub> (t)	q <sub>1</sub> (t+1)	q <sub>2</sub> (t+1)	
0	0	0	0	0	1
0	0	1	1	0	0
0	1	0	0	0	1
0	1	1	1	0	1
1	0	0	0	1	1
1	0	1	0	1	0
1	1	0	1	0	1
1	1	1	1	0	1

  - Possible states = { 00, 01, 10, 11 }  
→ 4 nodes in the diagram
- Possible Transitions = #rows in table  
→ 8 edges in the diagram





Reads as:

When at state **Q1** with output **Z1** and apply input **X**, we proceed to state **Q2** with output **Z2**.

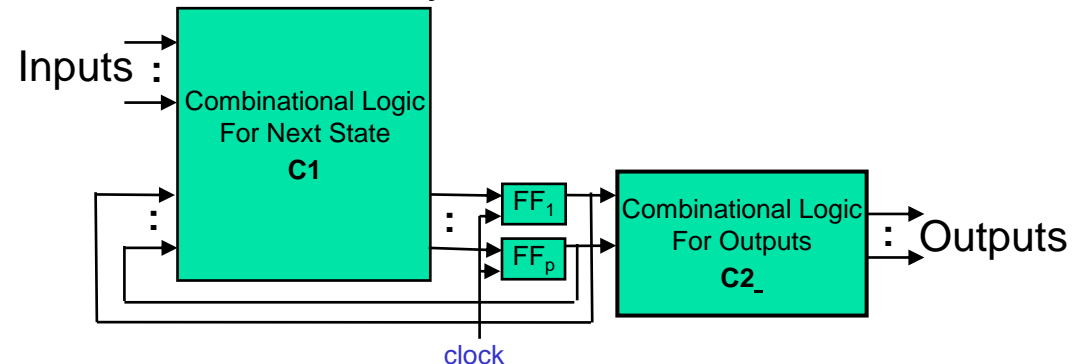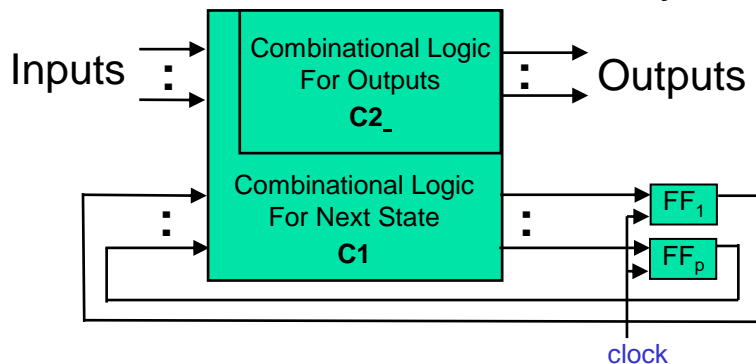
# Comparison of *Mealy* and *Moore* Machines

- Mealy Machines tend to have less states
  - Different outputs on arcs rather than on states
- Mealy Machines react faster to inputs
  - React in same cycle – don't need to wait for clock.
  - In Moore machines, more logic may be necessary to decode state into outputs – more gate delays after.
- Moore Machines are safer to use
  - Outputs change at clock edge (always one cycle later).
  - In Mealy machines, input change can cause output change as soon as logic is done – a big problem when two machines are interconnected – asynchronous feedback may occur.




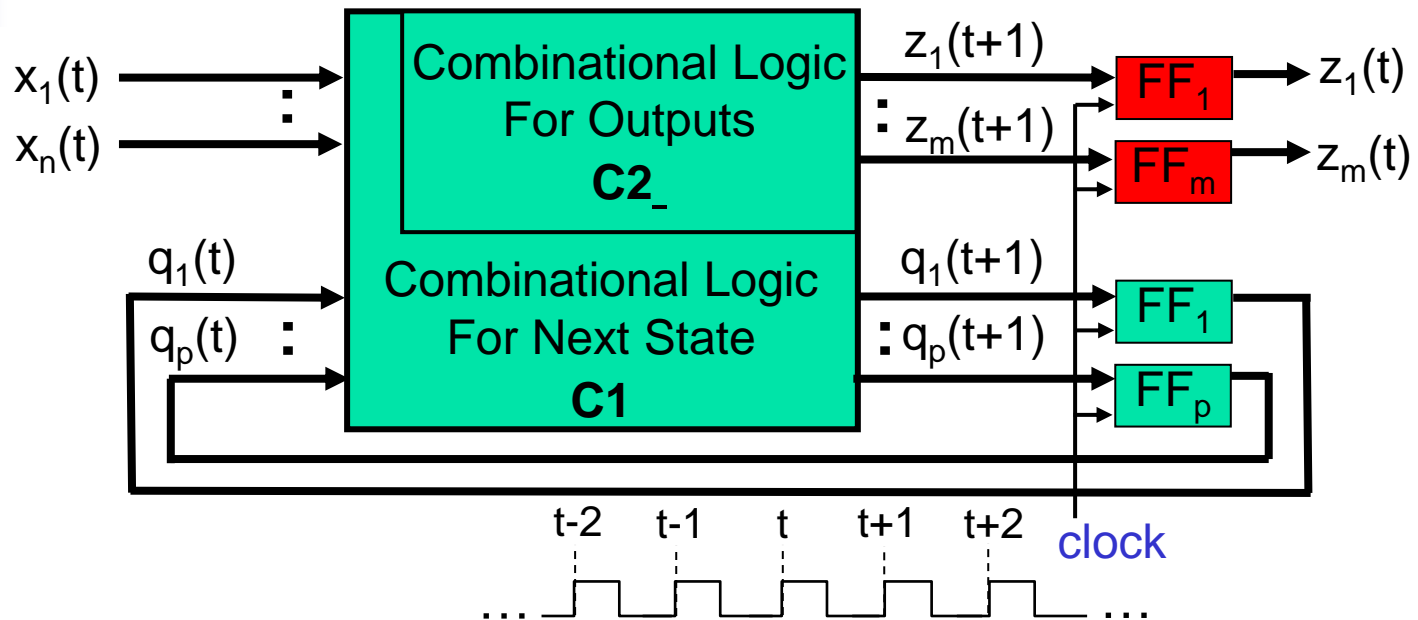
# Registered *Mealy* Machine (Really Moore)



- Synchronous (or registered) Mealy Machine
  - Registered outputs
  - Avoids “glitchy” outputs
- Registered Mealy Machine is actually Moore Machine. Why?
  - View outputs as expanded state vector
- So, we get Moore Machine with no output decoding